



BITS Pilani
Pilani Campus

Microwave Engineering (ECE F331)

Prof. Pankaj Arora
Department of Electrical and Electronics Engineering



BITS Pilani
Pilani Campus

Electromagnetic Fields and Microwave Engineering (ECE F314)

Prof. Pankaj Arora
Department of Electrical and Electronics Engineering

Course Handout



Course Description:

Course No.

Course Title

Instructor-in-charge

: ECE F314 or ECE F331

**: Electromagnetic Fields and
Microwave Engineering**

: Prof. Pankaj Arora

(email: pankaj.arora@pilani.bits-pilani.ac.in)

(Chamber: 2210-C, EEE Dept.)

: Prof. Dinesh Rano

Instructors (For Tutorials) :

sec-1: Prof. Dinesh Rano : Room 6102

sec-2: Prof. Pankaj Arora : Room 1202

Text Books:

- 1) TB1: David Pozar, “Microwave Engineering”, 4th edition, John Wiley & Sons, 2012.
- 2) TB2: John D. Kraus and Daniel A. Fleisch, “Electromagnetics”, 5th ed., McGraw-Hill, New York, 1999.

Reference Books:

- i) RB1: David K. Cheng, “Field and Wave Electromagnetics” 2nd ed. Pearson Education, New Delhi, 2009.
- ii) RB2: Samuel Y. Liao, “Microwave devices and circuits,” 3rd ed. , PHI 2008.
- iii) RB3: J. D. Krauss et al., “Antennas and Wave Propagation”, 4th edition, TMH 2010.

Evaluation Scheme (ECE F314):

Component	Duration	Marks (200)	Weightage	Evaluation type
Mid-term Test	90 min	60	30%	Closed Book
Quizzes	TBA	60	30%	Closed Book
Comprehensive Examination	3 hours	80	40%	OB + CB

Evaluation Scheme (ECE F331):

Component	Duration	Marks (200)	Weightage	Evaluation type
Mid-term Test	90 min	60	30%	Closed Book
Quizzes	TBA	30	15%	Closed Book
Lab	TBA	30	15%	Close/Open book
Comprehensive Examination	3 hours	80	40%	OB + CB

Why this course?



- Electrical Science, Microelectronic circuits, ADVD etc. (Amplifiers/Oscillators): Low frequency signal
- What about high frequency signal? Consequences ?

→ High frequency signals travel long distances

- For wireless communication: less height of antennas
- To destroy enemies' drones, radars etc. using high frequency signal
- Heating using high frequency signals e.g. Microwave, Oven
- Fusion heating to provide kinetic energy with high frequency signal
- Cargos scanners with high frequency signals
- Medical technologies: for cancer tumors
- Crowd Controls with high frequency signals

What we are going to learn in this course?



- How to generate high frequency signals? {Oscillators??}
- Or
- How to generate high frequency-high power signals?
- How to transmit high frequency signals? {Copper wires??}
- How to radiate high frequency signals? {Antenna??}

Course Content:



- Transmission Lines and Graphical Analysis
- EM Waves and Waveguides
- Microwave Generation and Amplification
- Antennas

Transmitting the signal from Point A to B (Transmission Lines)


e.g.: Power lines (Copper wires-50 Hz), Telephone Lines(Twisted paired wires-8 to 20kHz), TV Cables (Co-axial wires-MHz), Internet lines (Optical fibers-THz)

Main Difference: Frequency of operation
{Change in Medium}


Examples of Transmission Lines:




Cross-sectional view

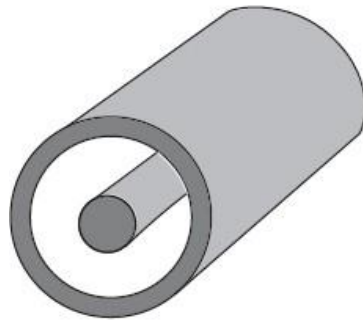


(a)

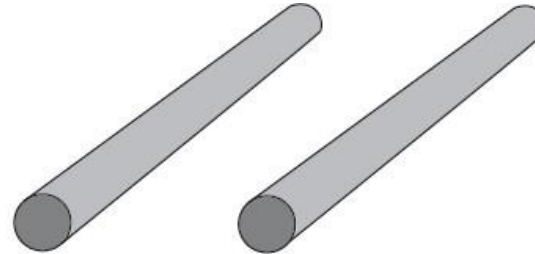


(b)

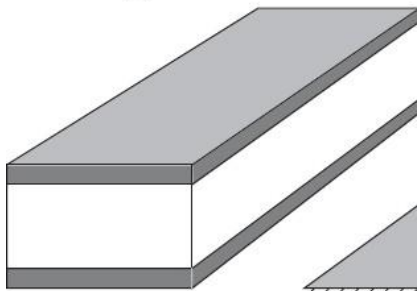

(c)

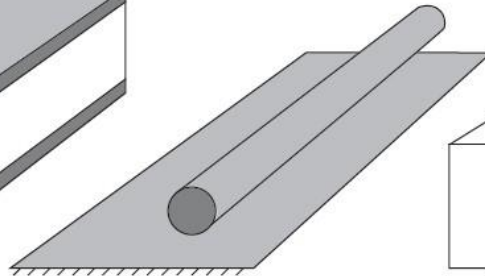

(d)

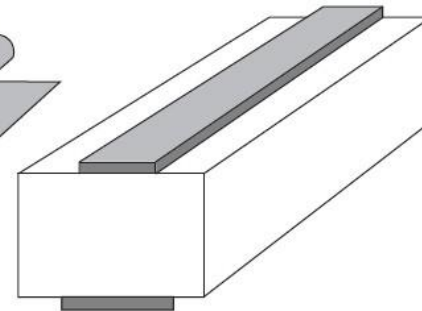

(e)






Typical transmission lines in cross-sectional view: (a) coaxial line, (b) two-wire line, (c) planar line, (d) wire above conducting plane, (e) microstrip line.

Example




A transmission line can be defined as a device for propagating or guiding energy from one point to another.

Transit time

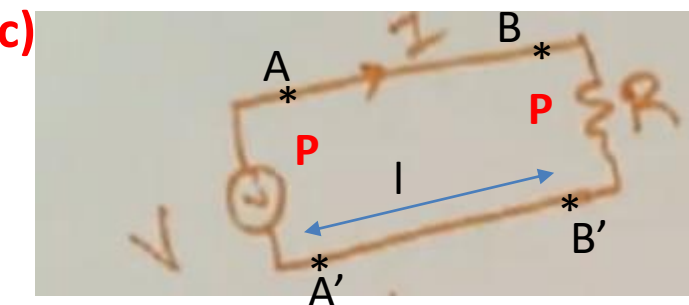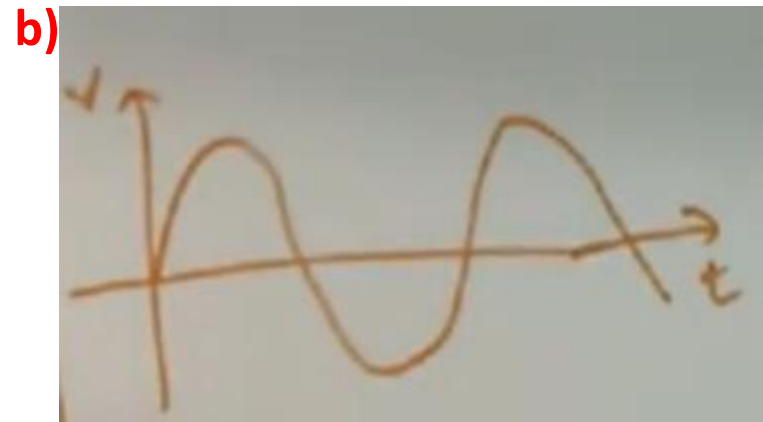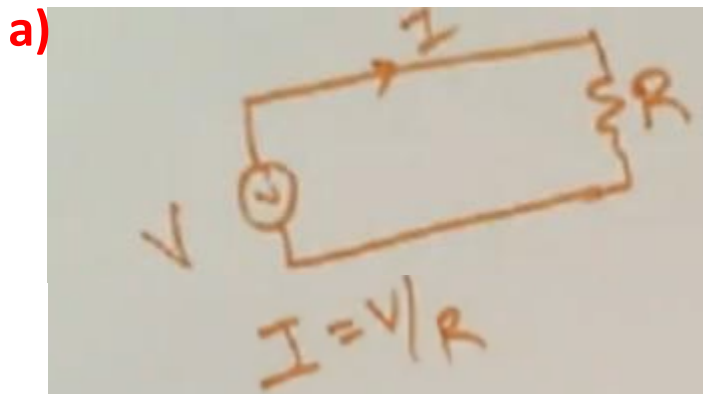

$$V - \alpha - IR - \alpha = 0$$

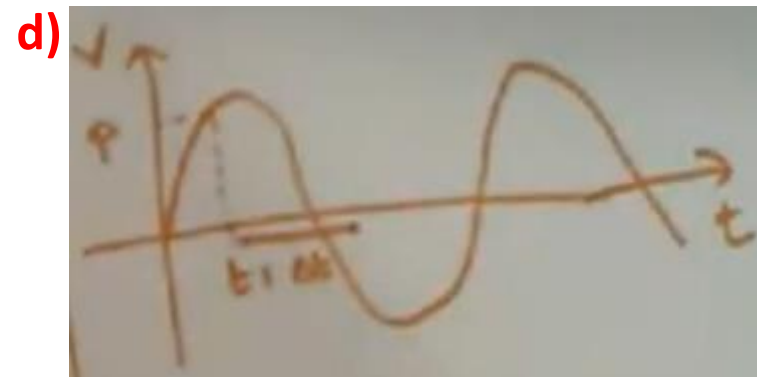


Value of Δt plays important role

High Frequency and longer lines : Circuit theory X


Response of parameters wrt frequency



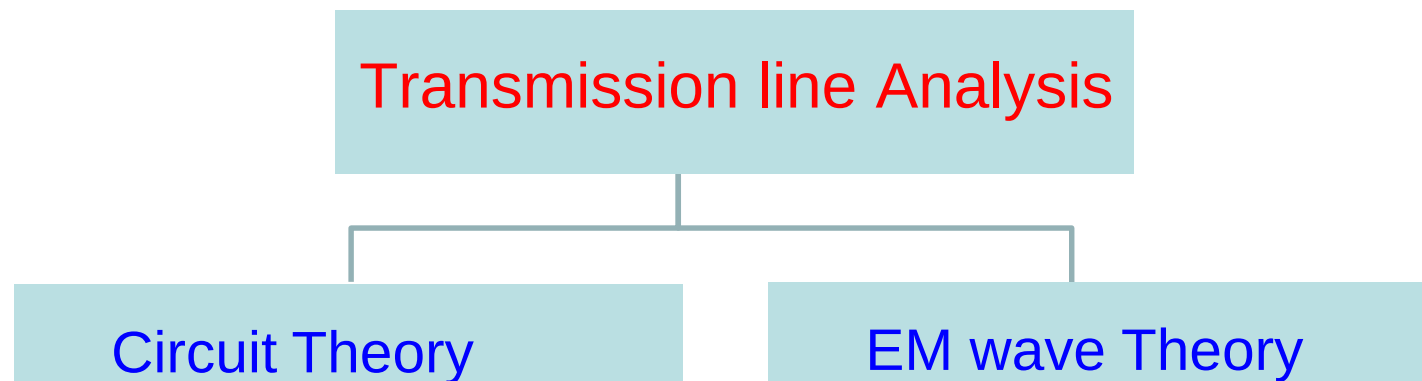- **At low frequencies**, the circuit elements are lumped since voltage and current waves affect the entire circuit at the same time.
- **At microwave frequencies**, such treatment of circuit elements is not possible since voltage and current waves do not affect the entire circuit at the same time.



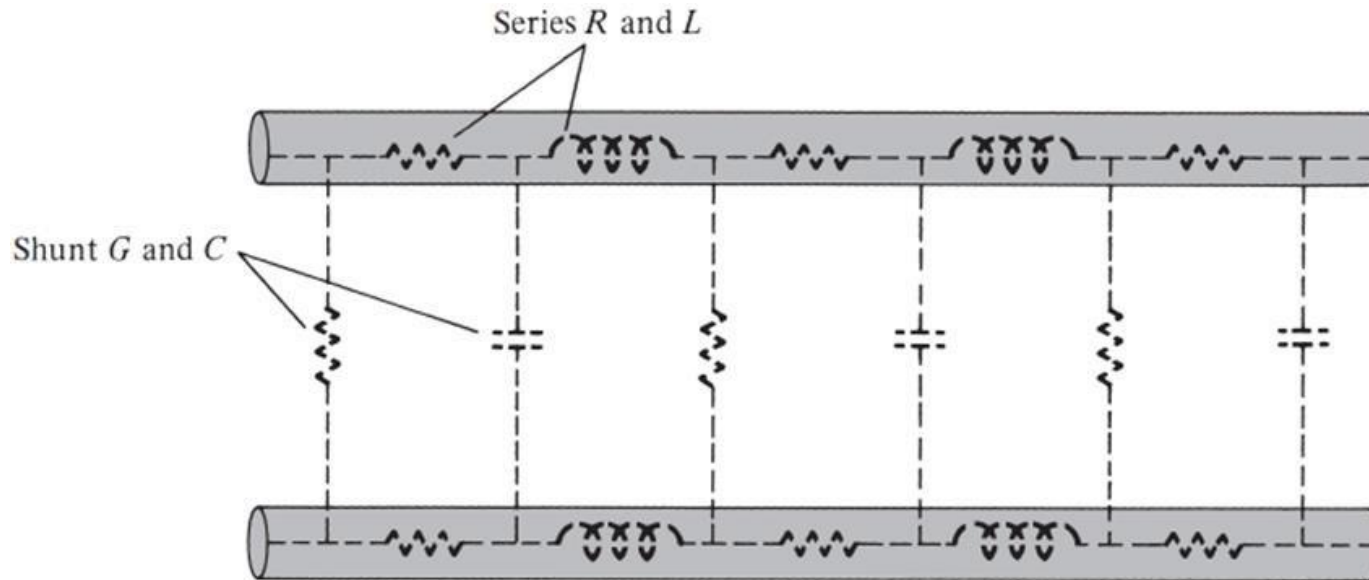Distributed parameters of a two-conductor transmission line



The impedance parameters L , R , C , and G represent:

L = series inductance per unit length

R = series resistance per unit length

C = shunt capacitance per unit length

G = shunt conductance per unit length.

General Transmission-line Equations




The impedance parameters L , R , C , and G represent:

L = series inductance per unit length


R = series resistance per unit length

C = shunt capacitance per unit length

G = shunt conductance per unit length.

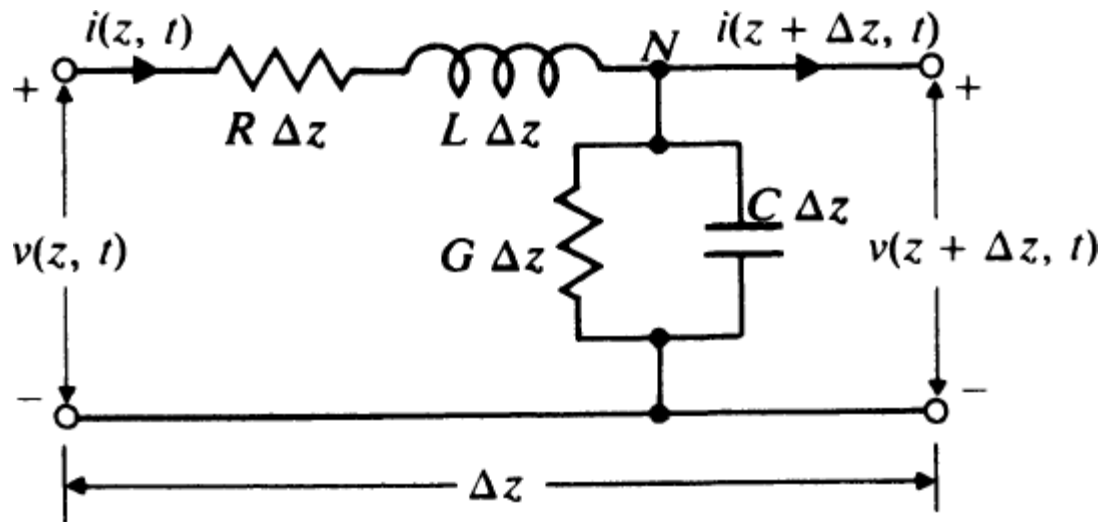

General Transmission-line Equations

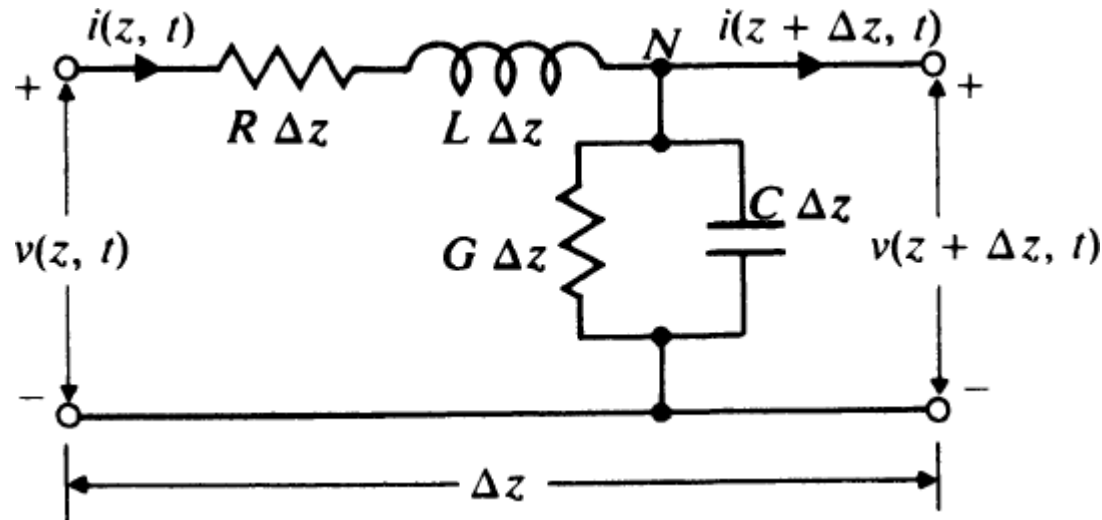


Kirchhoff's voltage law to the outer loop

$$V(z, t) = R \Delta z I(z, t) + L \Delta z \frac{\partial I(z, t)}{\partial t} + V(z + \Delta z, t)$$

$$\frac{V(z + \Delta z, t) - V(z, t)}{\Delta z} = R I(z, t) + L \frac{\partial I(z, t)}{\partial t}$$

General Transmission-line Equations

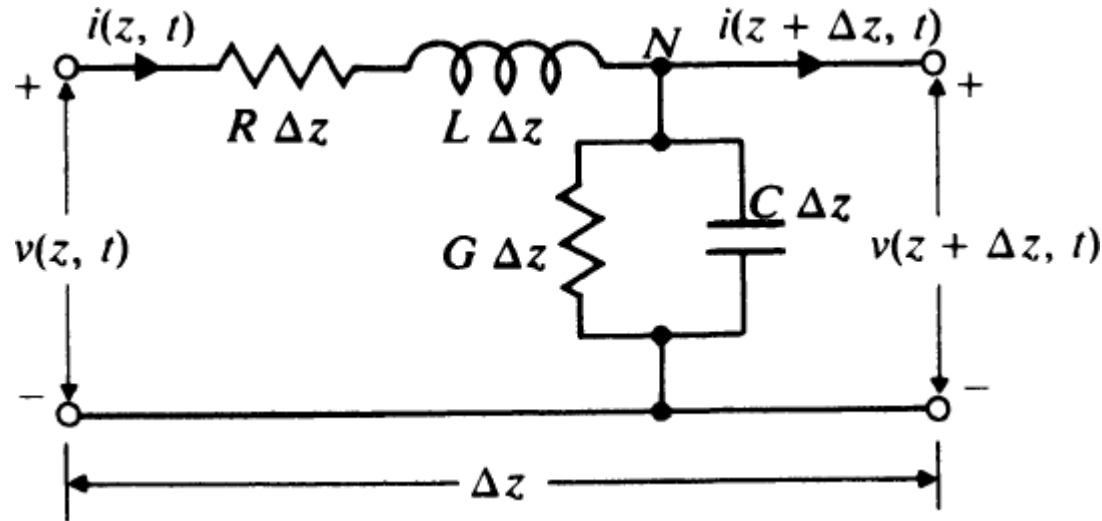

Kirchoff's current law

$$\begin{aligned}
 I(z, t) &= I(z + \Delta z, t) + \Delta I \\
 &= I(z + \Delta z, t) + G \Delta z V(z + \Delta z, t) + C \Delta z \frac{\partial V(z + \Delta z, t)}{\partial t}
 \end{aligned}$$

or

$$\frac{I(z + \Delta z, t) - I(z, t)}{\Delta z} = G V(z + \Delta z, t) + C \frac{\partial V(z + \Delta z, t)}{\partial t}$$

General Transmission-line Equations



$$-\frac{\partial v(z, t)}{\partial z} = Ri(z, t) + L \frac{\partial i(z, t)}{\partial t}$$

$$-\frac{\partial i(z, t)}{\partial z} = Gv(z, t) + C \frac{\partial v(z, t)}{\partial t}$$

General
Transmission-line
Equations

For Time-Harmonic Dependence:

$$V(z, t) = \text{Re} [V_s(z) e^{j\omega t}]$$

$$I(z, t) = \text{Re} [I_s(z) e^{j\omega t}]$$

Across the line,
values of V and I
are different

$$-\frac{dV_s}{dz} = (R + j\omega L) I_s$$

$$-\frac{dI_s}{dz} = (G + j\omega C) V_s$$

Time-Harmonic
Transmission-line
Equations

General Transmission-line Equations

$$\begin{aligned}-\frac{dV(z)}{dz} &= (R + j\omega L)I(z), \\ -\frac{dI(z)}{dz} &= (G + j\omega C)V(z).\end{aligned}$$

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)} \quad (m^{-1})$$

$$\frac{d^2 V(z)}{dz^2} = \gamma^2 V(z)$$

$$\frac{d^2 I(z)}{dz^2} = \gamma^2 I(z),$$

Wave characteristic of an infinite Transmission line



The phasor voltage and current wave equations may be written as

$$\frac{d^2 V(z)}{dz^2} = \gamma^2 V(z)$$

$$\frac{d^2 I(z)}{dz^2} = \gamma^2 I(z),$$

The general solutions to the voltage and current wave equations are

$$\begin{aligned} V(z) &= V^+(z) + V^-(z) \\ &= V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}, \end{aligned}$$

$$\begin{aligned} I(z) &= I^+(z) + I^-(z) \\ &= I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}, \end{aligned}$$

+z-directed waves

-z-directed waves

Propagation constant:

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)} \quad (m^{-1})$$

Characteristic impedance



$$-\frac{dV(z)}{dz} = (R + j\omega L)I(z),$$

$$-\frac{dI(z)}{dz} = (G + j\omega C)V(z).$$

$$\begin{aligned} V(z) &= V^+(z) + V^-(z) \\ &= V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}, \end{aligned}$$

$$\begin{aligned} I(z) &= I^+(z) + I^-(z) \\ &= I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}, \end{aligned}$$

$$\frac{d}{dz} \left(V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \right) = - (R + j\omega L) \left(I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \right)$$

$$\underbrace{V_0^+ (-\gamma) e^{-\gamma z}} + \underbrace{(\gamma) V_0^- e^{\gamma z}} = - (R + j\omega L) \underbrace{I_0^+ e^{-\gamma z}} - (R + j\omega L) \underbrace{I_0^- e^{\gamma z}}$$

$$\frac{V_0^+}{I_0^+} = \frac{(R + j\omega L)}{\gamma} = - \frac{V_0^-}{I_0^-} \Rightarrow Z_0$$

Wave characteristic of an infinite Transmission line



Characteristic impedance:

The **characteristic impedance** Z_0 of the line is the ratio of positively traveling voltage wave to current wave at any point on the line.

$$Z_0 = \frac{V_o^+}{I_o^+} = -\frac{V_o^-}{I_o^-} = \frac{R + j\omega L}{\gamma} = \frac{\gamma}{G + j\omega C}$$

$$= \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

Propagation constant:

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)} \quad (m^{-1})$$

Secondary Constants:

Propagation constant

Characteristic impedance

Classification of Transmission lines



➤ **Lossless line** ($R = 0$ and $G = 0$)

A **transmission line** is said to be **lossless** if the conductors of the line are perfect ($\sigma_c \approx \infty$) and the dielectric medium separating them is lossless ($\sigma \approx 0$).

$$\alpha = 0, \quad \gamma = j\beta = j\omega \sqrt{LC}$$

$$u = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}} = f\lambda$$

$$X_o = 0, \quad Z_o = R_o = \sqrt{\frac{L}{C}}$$

Wave characteristic of Transmission line (lossless)



$$V(z) = V^+(z) + V^-(z) \\ = \boxed{V_0^+ e^{-\gamma z}} + V_0^- e^{\gamma z},$$

[For Time harmonic variation]

$$v(z) = V_0^+ e^{-\gamma z} e^{j\omega t} \\ = V_0^+ e^{-\alpha z} e^{-j\beta z} e^{j\omega t}$$

For lossless line $\alpha = 0$

$$V(z) = V_0^+ e^{j(\omega t - \beta z)} \text{ or } V_0^+ e^{-j(\beta z - \omega t)}$$

$$\underline{\underline{\text{Re}[v(z)] = V_0^+ \cos(\beta z - \omega t)}} \quad \text{Wave nature}$$

Wave characteristic of Transmission line (not lossless)



$$V(z) = V^+(z) + V^-(z) \\ = \underline{V_0^+ e^{-\gamma z}} + V_0^- e^{\gamma z},$$

$$v(z) = V_0^+ e^{-\alpha^2 - j\beta^2 z}$$

Time harmonic e

$$v(z) = V_0^+ e^{-\alpha z} e^{-j\beta z - \omega t}$$

What is $\beta \rightarrow ??$

units

What is $\alpha \rightarrow ??$

units

$$e^{-\alpha^2} \Rightarrow$$

$$[1 \text{ Np/m} = -8.68 \text{ dB}] ??$$

Classification of Transmission lines



➤ Distortionless line ($R/L=G/C$)

A **distortionless line** is one in which the attenuation constant α is frequency independent while the phase constant β is linearly dependent on frequency.

$$\begin{aligned}\gamma &= \sqrt{RG \left(1 + \frac{j\omega L}{R}\right) \left(1 + \frac{j\omega C}{G}\right)} \\ &= \sqrt{RG} \left(1 + \frac{j\omega C}{G}\right) = \alpha + j\beta\end{aligned}$$

$$\alpha = \sqrt{RG}, \quad \beta = \omega \sqrt{LC}$$

$$Z_o = \sqrt{\frac{R(1 + j\omega L/R)}{G(1 + j\omega C/G)}} = \sqrt{\frac{R}{G}} = \sqrt{\frac{L}{C}} = R_o + jX_o$$

$$R_o = \sqrt{\frac{R}{G}} = \sqrt{\frac{L}{C}}, \quad X_o = 0$$

$$u = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}} = f\lambda$$

Classification of Transmission lines



Low loss line ($R \ll \omega L$, $G \ll \omega C$)

$$\begin{aligned}\gamma &= \alpha + j\beta = j\omega\sqrt{LC}\left(1 + \frac{R}{j\omega L}\right)^{1/2}\left(1 + \frac{G}{j\omega C}\right)^{1/2} \\ &\cong j\omega\sqrt{LC}\left(1 + \frac{R}{2j\omega L}\right)\left(1 + \frac{G}{2j\omega C}\right) \\ &\cong j\omega\sqrt{LC}\left[1 + \frac{1}{2j\omega}\left(\frac{R}{L} + \frac{G}{C}\right)\right];\end{aligned}$$

$$\alpha \cong \frac{1}{2}\left(R\sqrt{\frac{C}{L}} + G\sqrt{\frac{L}{C}}\right)$$

$$\beta \cong \omega\sqrt{LC} \quad (\text{approximately a linear function of } \omega).$$

Classification of Transmission lines



Low loss line ($R \ll \omega L$, $G \ll \omega C$)

$$\alpha_p = \frac{\omega}{\beta} \cong \frac{1}{\sqrt{LC}}$$

$$Z_0 = R_0 + jX_0 = \sqrt{\frac{L}{C}} \left(1 + \frac{R}{j\omega L}\right)^{1/2} \left(1 + \frac{G}{j\omega C}\right)^{-1/2}$$

$$\cong \sqrt{\frac{L}{C}} \left[1 + \frac{1}{2j\omega} \left(\frac{R}{L} - \frac{G}{C}\right)\right];$$

$$R_0 \cong \sqrt{\frac{L}{C}}$$

$$X_0 \cong -\sqrt{\frac{L}{C}} \frac{1}{2\omega} \left(\frac{R}{L} - \frac{G}{C}\right)$$

Reflection coefficient



The general solutions to the voltage and current wave equations are


$$V(z) = V^+(z) + V^-(z)$$

$$I(z) = I^+(z) + I^-(z) \quad ;$$

$$= I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z},$$

$$V_s(z) = V_o^+ e^{-\gamma z} + V_o^- e^{\gamma z}$$
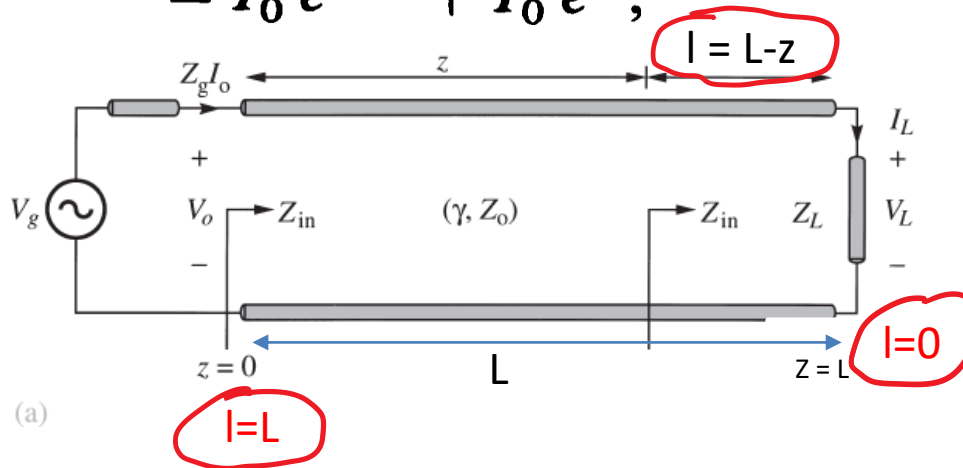
$$I_s(z) = \frac{V_o^+}{Z_o} e^{-\gamma z} - \frac{V_o^-}{Z_o} e^{\gamma z}$$



$$Z_{in} = \frac{V_s(z)}{I_s(z)} = Z_o \frac{V_o^+ e^{-\gamma z} + V_o^- e^{\gamma z}}{V_o^+ e^{-\gamma z} - V_o^- e^{\gamma z}}$$

**Voltage reflection coefficient
(at load, l)**

$$\Gamma(l) = \frac{V_o^- e^{-\gamma l}}{V_o^+ e^{\gamma l}} \approx \frac{V_o^-}{V_o^+} e^{-2\gamma l} = \text{Reflection coefficient}$$

$$\left[\begin{aligned} V_s(l) &= V_o^+ e^{-\gamma l} + V_o^- e^{\gamma l} \\ I_s(l) &= \frac{V_o^+}{Z_o} e^{-\gamma l} - \frac{V_o^-}{Z_o} e^{\gamma l} \end{aligned} \right]$$

Reflection coefficient



$$\Gamma(l) = \frac{V_o^- e^{-\gamma l}}{V_o^+ e^{\gamma l}} \approx \frac{V_o^-}{V_o^+} e^{-2\gamma l} = \text{Reflection coefficient}$$

at $l=0$ $\left[\Gamma_{l=0} = \frac{V_o^-}{V_o^+} \right]$

So $\left[\Gamma(l) = (\Gamma_{l=0}) e^{-2\gamma l} \right] \Rightarrow \underline{\text{Important}}$

$$\left[\begin{aligned} V_s(l) &= V_o^+ e^{+\gamma l} + V_o^- e^{-\gamma l} \\ I_s(l) &= \frac{V_o^+}{Z_o} e^{+\gamma l} - \frac{V_o^-}{Z_o} e^{-\gamma l} \end{aligned} \right] \text{ So } Z(l) = \frac{V_s(l)}{I_s(l)}$$

$$\left[Z(l) = \left(\frac{V_o^+ e^{+\gamma l} + V_o^- e^{-\gamma l}}{V_o^+ e^{+\gamma l} - V_o^- e^{-\gamma l}} \right) Z_o \right]$$

Impedance on any point of transmission line



$$Z(l) = \frac{V_s(l)}{I_s(l)}$$

$$\left[Z(l) = \frac{V_0^+ e^{\gamma l} + V_0^- e^{-\gamma l}}{V_0^+ e^{\gamma l} - V_0^- e^{-\gamma l}} Z_0 \right] \Rightarrow Z(l) = Z_0 \frac{V_0^+ e^{\gamma l} \left[1 + \frac{V_0^-}{V_0^+} e^{-2\gamma l} \right]}{V_0^+ e^{\gamma l} \left[1 - \frac{V_0^-}{V_0^+} e^{-2\gamma l} \right]}$$

$$S. \quad Z(l) = Z_0 \frac{[1 + \Gamma(l)]}{[1 - \Gamma(l)]}$$

$$Z(l) = Z_0 \frac{[1 + \Gamma(l)]}{[1 - \Gamma(l)]}$$

$$\Gamma(l) = \frac{Z(l) - Z_0}{Z(l) + Z_0}$$

Imp. at load $l=0$

$$\Gamma(0) = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Characteristics of transmission line



$$Z(l) = Z_0 \left[\frac{1 + \Gamma(l)}{1 - \Gamma(l)} \right] \quad \cdot \quad \Gamma(l) = \frac{V_0^-}{V_0^+} e^{-2\gamma l}$$

$$\Gamma(l) = \frac{Z(l) - Z_0}{Z(l) + Z_0}$$

$$\Gamma_{l(l=0)} = \frac{V_0^-}{V_0^+}$$

$$\Gamma_{l \text{ at } l=0} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

at $l=0$


$$Z_L = \frac{Z_0(1 + \Gamma_l)}{(1 - \Gamma_l)}$$

$$0 \leq |\Gamma| \leq 1$$

Characteristics of transmission line



Cases:

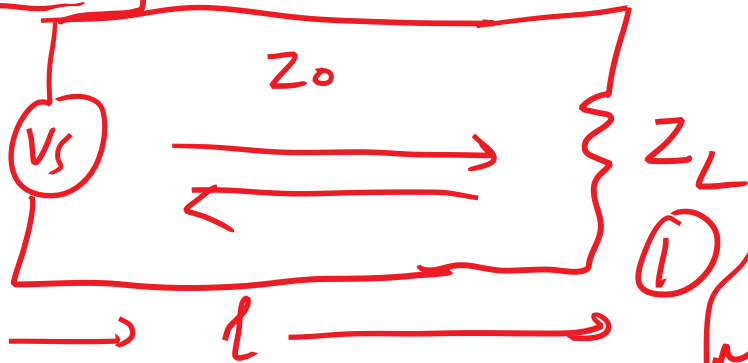

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \quad Z_L = Z_0$$

$$\Gamma_L = 0 \quad \checkmark$$

No reflection

matched line

②


Infinite line

$$\Gamma(l) = \Gamma_L e^{-2\gamma l}$$

$$= \Gamma_L e^{-2\alpha l - j\beta l}$$

There will be no reflection

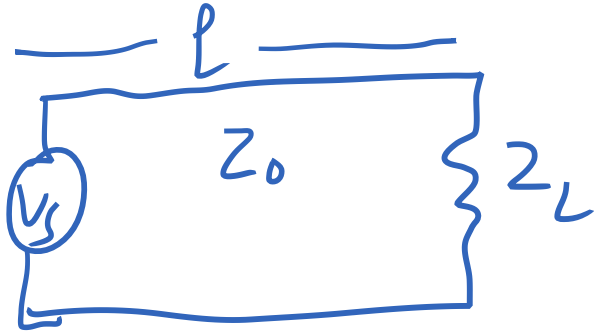Wave characteristic of finite Transmission line



$$Z(l) = Z_0 \left[\frac{1 + \Gamma(l)}{1 - \Gamma(l)} \right]$$

$$\Gamma(l) = \Gamma_0 e^{-2\gamma l}$$

$$\Gamma_0 = \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right)$$

$$Z(l) = Z_0 \left[\frac{1 + \frac{Z_L - Z_0}{Z_L + Z_0} e^{-2\gamma l}}{1 - \frac{Z_L - Z_0}{Z_L + Z_0} e^{-2\gamma l}} \right]$$

Wave characteristic of finite Transmission line



$$Z(l) = Z_0 \left[1 + \frac{Z_L - Z_0}{Z_L + Z_0} e^{-2\gamma l} \right] \left[1 - \frac{Z_L - Z_0}{Z_L + Z_0} e^{-2\gamma l} \right]$$

$$Z(l) = Z_0 \left[\frac{(Z_L + Z_0) + (Z_L - Z_0) e^{-2\gamma l}}{(Z_L + Z_0) - (Z_L - Z_0) e^{-2\gamma l}} \right]$$

$$Z(l) = Z_0 \left[\frac{Z_L (e^{\gamma l} + e^{-\gamma l}) + Z_0 (e^{\gamma l} - e^{-\gamma l})}{Z_L (e^{\gamma l} - e^{-\gamma l}) + Z_0 (e^{\gamma l} + e^{-\gamma l})} \right]$$

Wave characteristic of finite Transmission line



$$Z(l) = Z_0 \left[\frac{Z_L (e^{\gamma l} + e^{-\gamma l}) + Z_0 (e^{\gamma l} - e^{-\gamma l})}{Z_L (e^{\gamma l} - e^{-\gamma l}) + Z_0 (e^{\gamma l} + e^{-\gamma l})} \right]$$

$$Z(l) = Z_0 \left[\frac{Z_L \cosh(\gamma l) + Z_0 \sinh(\gamma l)}{Z_0 \cosh(\gamma l) + Z_L \sinh(\gamma l)} \right]$$

$$Z(l) = Z_0 \left[\frac{Z_L + Z_0 \tanh(\gamma l)}{Z_0 + Z_L \tanh(\gamma l)} \right] \text{ Imp.}$$


Input impedance at any point along a general (lossy) transmission line

Wave characteristic of finite Transmission line



$$Z_{in} = Z_o \left[\frac{Z_L + jZ_o \tan \beta l}{Z_o + jZ_L \tan \beta l} \right]$$

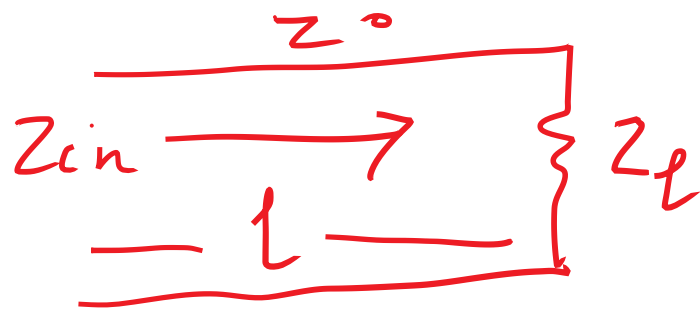for lossless transmission line $\alpha = 0$



$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o}$$


$$\Gamma(l) = \Gamma_L e^{-2\gamma l}$$

$$Z(l) = Z_o \left[\frac{1 + \Gamma(l)}{1 - \Gamma(l)} \right]$$

$$Z_{in} = Z_o \left[\frac{Z_L + Z_o \tanh \gamma l}{Z_o + Z_L \tanh \gamma l} \right]$$

βl ??

Example-1

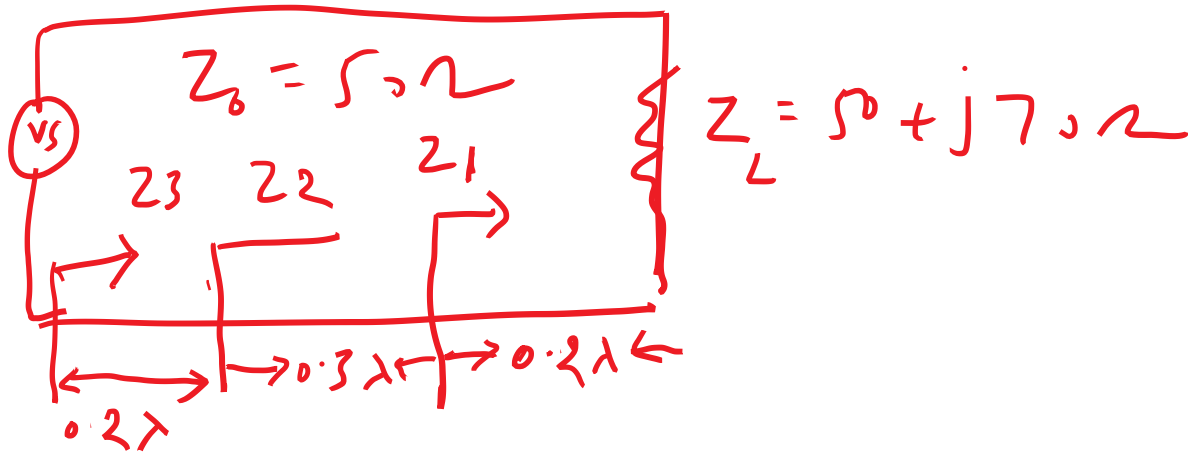

Find out $Z_1 = ?$

$Z_2 = ?$

$Z_3 = ?$

Reflection Coefficient & VSWR



$$\Gamma(l) = \frac{Z(l) - Z_0}{Z(l) + Z_0} \quad \text{at } l=0$$
$$\Gamma_l = \frac{Z_l - Z_0}{Z_l + Z_0}$$
$$\Gamma_l = \frac{V_0^-}{V_0^+} \quad \Gamma(l) = \frac{V_0^-}{V_0^+} e^{-2\gamma l}$$

Measure of the mismatch of a line can be done by calculating standing wave ratio (SWR)-s

$$S = \frac{|V_{\max}|}{|V_{\min}|} = \frac{1 + |\Gamma|}{1 - |\Gamma|} \quad (\text{Dimensionless}).$$

$$|\Gamma| = \frac{S - 1}{S + 1} \quad (\text{Dimensionless}).$$

Reflection Coefficient & VSWR



$$\Gamma = \frac{Z_L - Z_o}{Z_L + Z_o}$$

$$|\Gamma| = \frac{S - 1}{S + 1}$$

$$\left[S = \frac{1 + |\Gamma|}{1 - |\Gamma|} \right]$$

$\Gamma = 0, \quad S = 1$ when $Z_L = Z_o$ (Matched load);

$\Gamma = -1, \quad S \rightarrow \infty$ when $Z_L = 0$ (Short circuit);

$\Gamma = +1, \quad S \rightarrow \infty$ when $Z_L \rightarrow \infty$ (Open circuit).

what is value of $|\Gamma|$??
if load is inductive or capacitive

$$V = V^+ e^{j\beta l} + V^- e^{-j\beta l} \text{ lossless line}$$

$$V = V^+ e^{j\beta l} + V^- e^{-j\beta l}$$

$$V = V^+ e^{j\beta l} \left(1 + \frac{V^-}{V^+} e^{-j2\beta l} \right)$$

$$V = V^+ e^{j\beta l} \left(1 + \Gamma_L e^{-j2\beta l} \right)$$

$$V = V^+ e^{j\beta l} \left(1 + |\Gamma_L| e^{j\phi} e^{-j2\beta l} \right)$$

$$|V| = |V^+| \left| 1 + |\Gamma_L| e^{j(\phi - 2\beta l)} \right|$$

$$\text{for } V_{\max} \rightarrow |e^{j(\phi - 2\beta l)}| = 1$$

$I_{\min}$

$$\text{For } V_{\min}: \\ |e^{j(\phi - 2\beta l)}| = -1$$

$$\phi - 2\beta l = (2n+1)\pi$$

$I_{\max}$

$$\text{So } \phi - 2\beta l = 2n\pi$$

Rmax and Rmin



$$V_{max} = V^+ (1 + \Gamma_L)$$

$$I_{min} = \frac{V^+}{Z_0} (1 - \Gamma_L)$$

$$V_{min} = V^+ (1 - \Gamma_L)$$

$$I_{max} = \frac{V^+}{Z_0} (1 + \Gamma_L)$$

$$\text{So } R_{max} = Z_0 \left(\frac{1 + \Gamma_L}{1 - \Gamma_L} \right)$$

$$R_{min} = \frac{Z_0}{\left(\frac{1 + \Gamma_L}{1 - \Gamma_L} \right)}$$

$$\text{So } \underline{R_{max} = Z_0 (VSWR)}$$

$$R_{min} = \frac{Z_0}{VSWR}$$

Example



$$Z_{in} = \frac{Z_0 (Z_L + j Z_0 \tan \beta L)}{(Z_0 + j Z_L \tan \beta L)}$$

a) find Z_{in} at $l = \frac{\lambda}{2}$ and $l = \frac{\lambda}{4}$?



at $l = \lambda/2$

$$Z_{in} = Z_L$$

at $l = \lambda/4$

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

Example

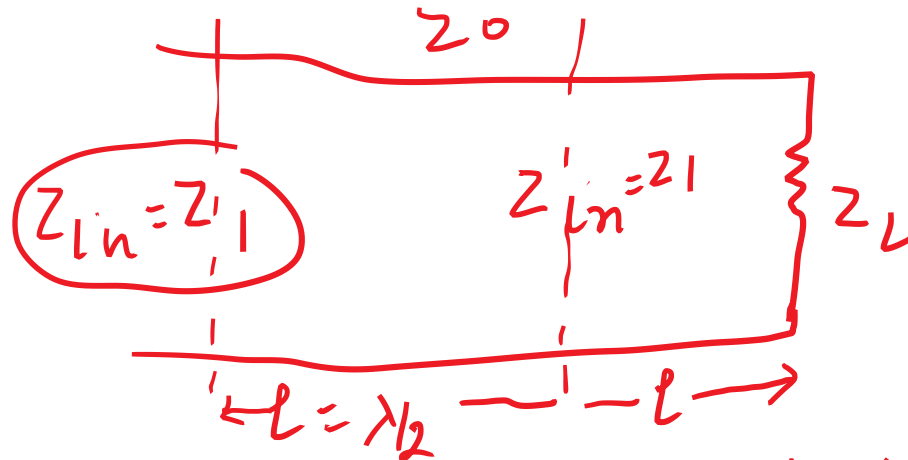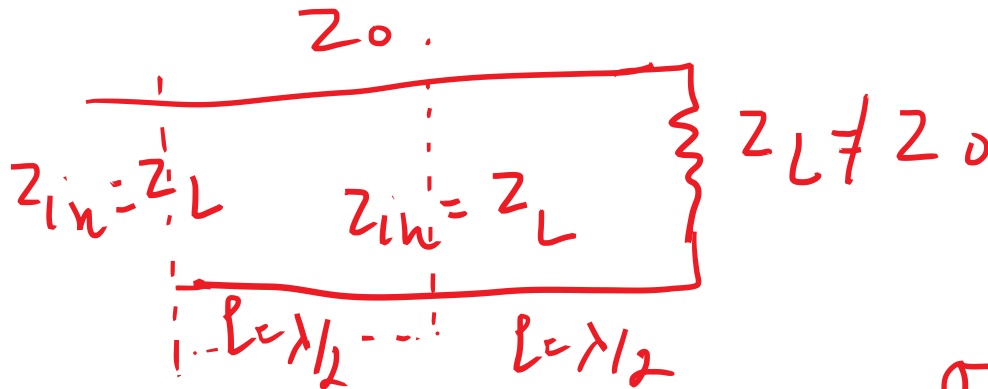

at $l = \lambda/2$

$$Z_{in} = Z_L$$

$\Rightarrow$ Impedance repeats at every distance $= \frac{\lambda}{2}$

Example-2



$$Z_0 = 50 \Omega$$

$$Z_L = 75 - 75j \Omega$$

Calculate a) Γ_L , VSWR

$$\text{VSWR} = 3.34$$

$$\Gamma_L = 0.54 \angle -40.6^\circ$$

$$\Gamma(0.2\lambda) = 0.54 \angle +175.4^\circ$$

$$Z(0.2\lambda) = (14.95 + j1.82) \Omega$$

$$\Gamma(0.3\lambda) = 0.54 \angle 103.39^\circ$$

$$Z(0.3\lambda) = (22.83 + j34.136) \Omega$$

b) $Z_{in}(0.2\lambda)$, $\Gamma_{in}(0.2\lambda)$

c) $Z_{in}(0.3\lambda)$, $\Gamma_{in}(0.3\lambda)$

d) $Z_{in}(0.7\lambda)$, $\Gamma_{in}(0.7\lambda)$

e) Location of V_{max} & V_{min} -

Example-2



Location of $V_{\max} \approx I_{\min} \approx R_{\max}$

$$\phi - 2\beta l = 2n\pi \quad n=1$$

$$-40.6^\circ - 2\beta l = 360^\circ$$

$$-2\beta l = 400.6^\circ$$

$$-l = \frac{400.6}{2 \times 2 \times 180} \lambda$$


$$l = -0.55\lambda + 0.5\lambda + 0.5\lambda = 0.45\lambda$$

maxima ↑

minima

impedance repeats at every $\lambda/2$ length

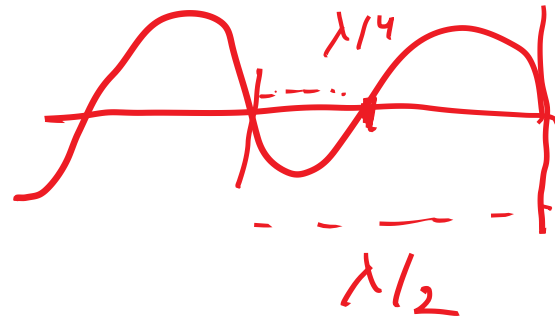
$$\rightarrow 0.45\lambda - 0.25\lambda = \boxed{0.20\lambda}$$




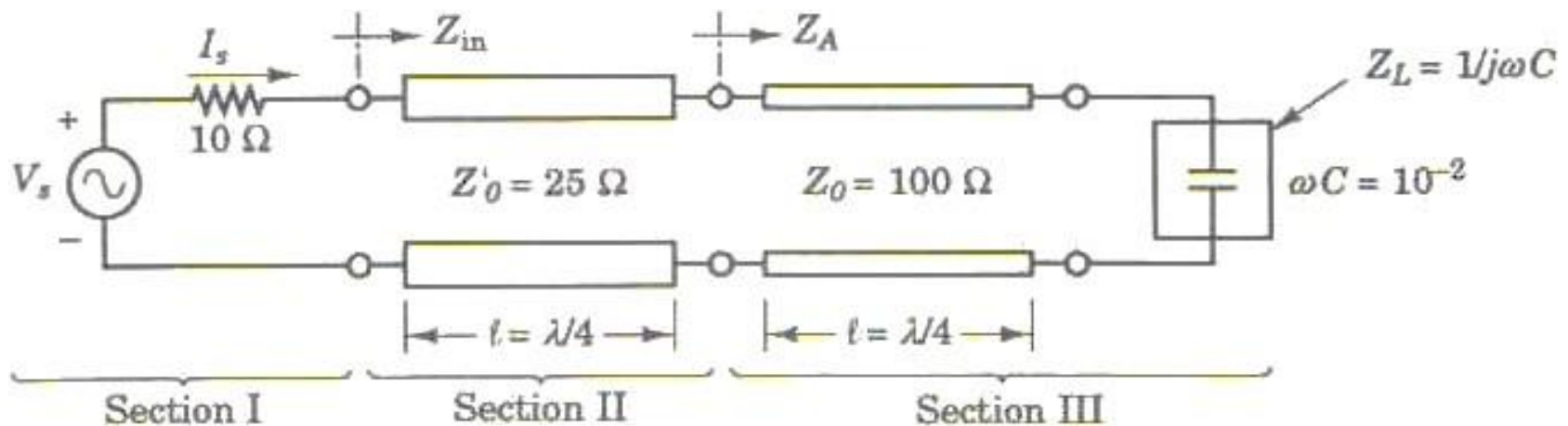Example-2



What is the input impedance supplied by the source?



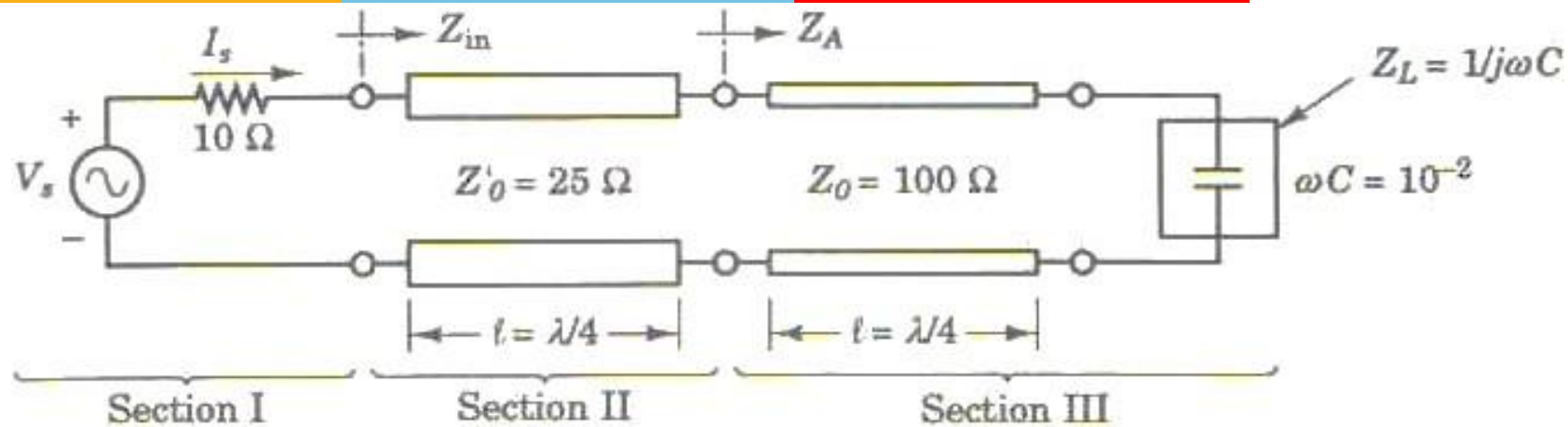

$$Z_i = Z_o \left[\frac{Z_L + jZ_o \tan \beta l}{Z_o + jZ_L \tan \beta l} \right]$$

$$Z_{\lambda/4} = \frac{Z_o^2}{Z_L}$$

Transmission Lines as circuit elements




For a lossless line:

$$Z_{in} = Z_o \left[\frac{Z_L + jZ_o \tan \beta l}{Z_o + jZ_L \tan \beta l} \right]$$

Transmission Lines terminated in short or open circuits are commonly used as tuning elements.

If the line is **short-circuited**: $Z_L = 0$

$$Z_{SC} = jZ_o \tan \beta l$$

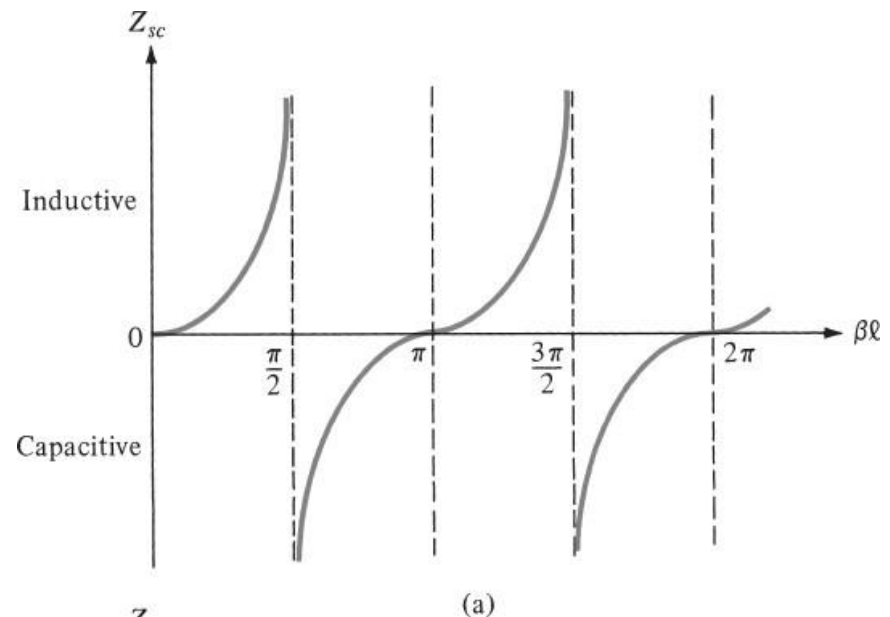

Transmission Lines as circuit elements



$$Z_{sc} = jZ_0 \tan \beta l$$

$$\text{if } \beta l < \pi/2 \\ l < \frac{\lambda}{4}$$

$$\tan \beta l \approx \beta l$$

$$Z_{sc} = jZ_0 \beta l$$

$$Z_{sc} = j\sqrt{\frac{L}{C}} \omega \sqrt{LC} \cdot l = j\omega L l = \underbrace{j\omega L}_{\text{Inductor}} \Rightarrow$$

$$\pi/2 < \beta l < \pi \rightarrow \text{Capacitor}$$

$$\text{at } \beta l = \pi/2 \rightarrow Z_{sc} = \infty \rightarrow \text{capacitor} \checkmark$$


Transmission Lines as circuit elements



For a lossless line: open-circuited:

$$Z_i = Z_o \left\{ \frac{Z_L + jZ_o \tan \beta l}{Z_o + jZ_L \tan \beta l} \right\}$$

$$Z_{in} = -jZ_o \cot \beta l$$

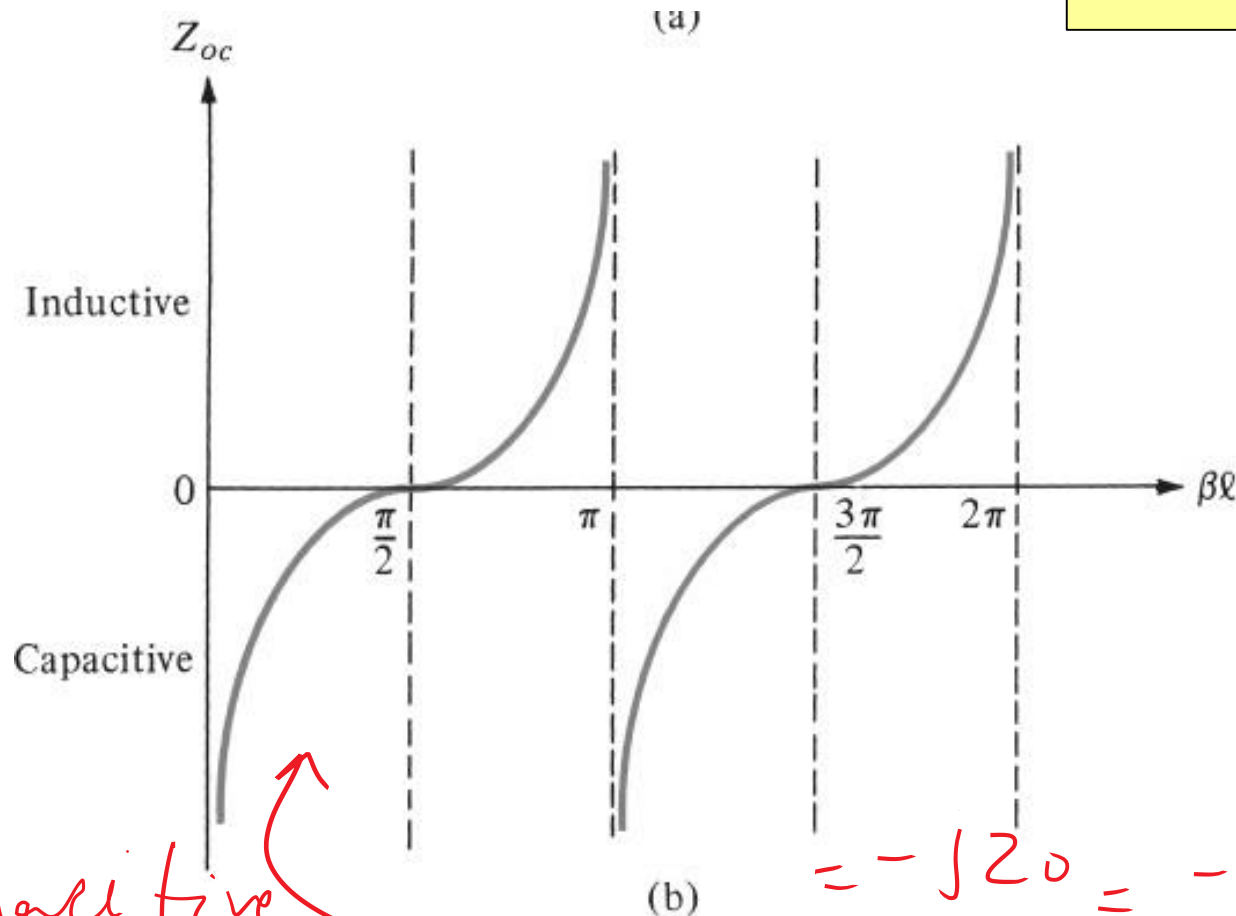

$$\beta l < \frac{\pi}{2}$$

$$l < \frac{\lambda}{4}$$

$$= -jZ_o \tan \beta l$$

$$= -jZ_o = -j\sqrt{L/C} = \left[\frac{1}{j\omega C} \right]$$

Capacitive

Transmission Lines as circuit elements



$$Z_{sc} = jZ_0 \tan \beta l$$

$$Z_{oc} = -jZ_0 \cot \beta l = \frac{Z_0}{j \tan \beta l}$$

$$Z_0 = \sqrt{Z_{oc} Z_{sc}}$$

$$Z_0 = \sqrt{Z_{OC} Z_{SC}}$$
$$\gamma = \frac{1}{l} \tanh^{-1} \sqrt{\frac{Z_{SC}}{Z_{OC}}}$$

$$\frac{Z_{sc}}{Z_{oc}} = \tan^2 \beta l$$

$$\beta = \frac{1}{l} \tan^{-1} \sqrt{\frac{Z_{sc}}{Z_{oc}}}$$

Lossy line

Smith Chart



Transmission line calculation-such as the determination of input impedance, reflection coefficient and load impedance often involve tedious manipulations of complex numbers.

Graphical method of solution → **Smith Chart**

Smith Chart was devised by P.H.Smith (in 1930).


Smith Chart is a graphical plot of normalized resistance and reactance functions in the reflection-coefficient plane

Reflection Co-efficient plane (Finite plane)



$$\left[\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \right]$$

Z_0 normalized impedance

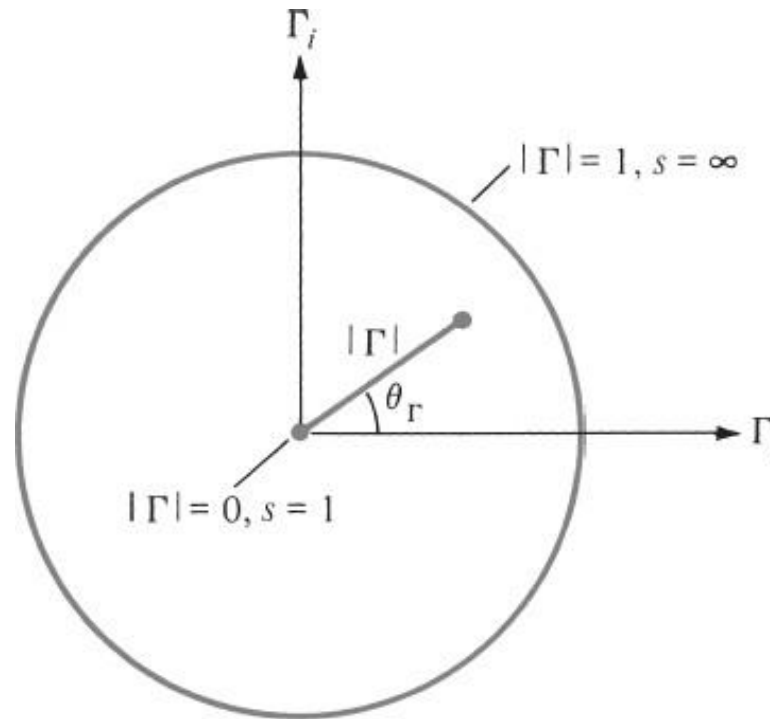

What
about
Z impedance
plane??
==

The **normalized impedance** is represented on the **Smith chart** by using families of curves that identify the **normalized resistance** r (real part) and the **normalized reactance** x (imaginary part)

Smith Chart Circle Equations



- If a lossless line of Z_0 is terminated with Z_L ,
 $z_L = Z_L/Z_0$ (normalized load impedance),

$$\Gamma = \frac{z_L - 1}{z_L + 1} = |\Gamma| e^{j\theta} \quad \longrightarrow \quad z_L = \frac{1 + |\Gamma| e^{j\theta}}{1 - |\Gamma| e^{j\theta}}$$

- Let $\Gamma = \Gamma_r + j\Gamma_i$, and $z_L = r_L + jx_L$.

$$r_L + jx_L = \frac{(1 + \Gamma_r) + j\Gamma_i}{(1 - \Gamma_r) - j\Gamma_i} \quad \longrightarrow \quad r_L = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

$$x_L = \frac{2\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

$$\left(\Gamma_r - \frac{r_L}{1 + r_L} \right)^2 + \Gamma_i^2 = \left(\frac{1}{1 + r_L} \right)^2$$

r circle

$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x_L} \right)^2 = \left(\frac{1}{x_L} \right)^2$$

x circle

Smith Chart Circle Equations




$$\left(\Gamma_r - \frac{r_L}{1 + r_L} \right)^2 + \Gamma_i^2 = \left(\frac{1}{1 + r_L} \right)^2$$
$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x_L} \right)^2 = \left(\frac{1}{x_L} \right)^2$$

The result for the **real part** indicates that on the complex plane with coordinates $(\text{Re}(\Gamma), \text{Im}(\Gamma))$ all the possible impedances with a given normalized resistance r are found on a **circle** with

$$\text{Center} = \left\{ \frac{r}{1 + r}, 0 \right\} \qquad \text{Radius} = \frac{1}{1 + r}$$

As the normalized resistance r varies from **0** to ∞ , we obtain a family of circles completely contained inside the domain of the reflection coefficient $|\Gamma| \leq 1$.

r-circles

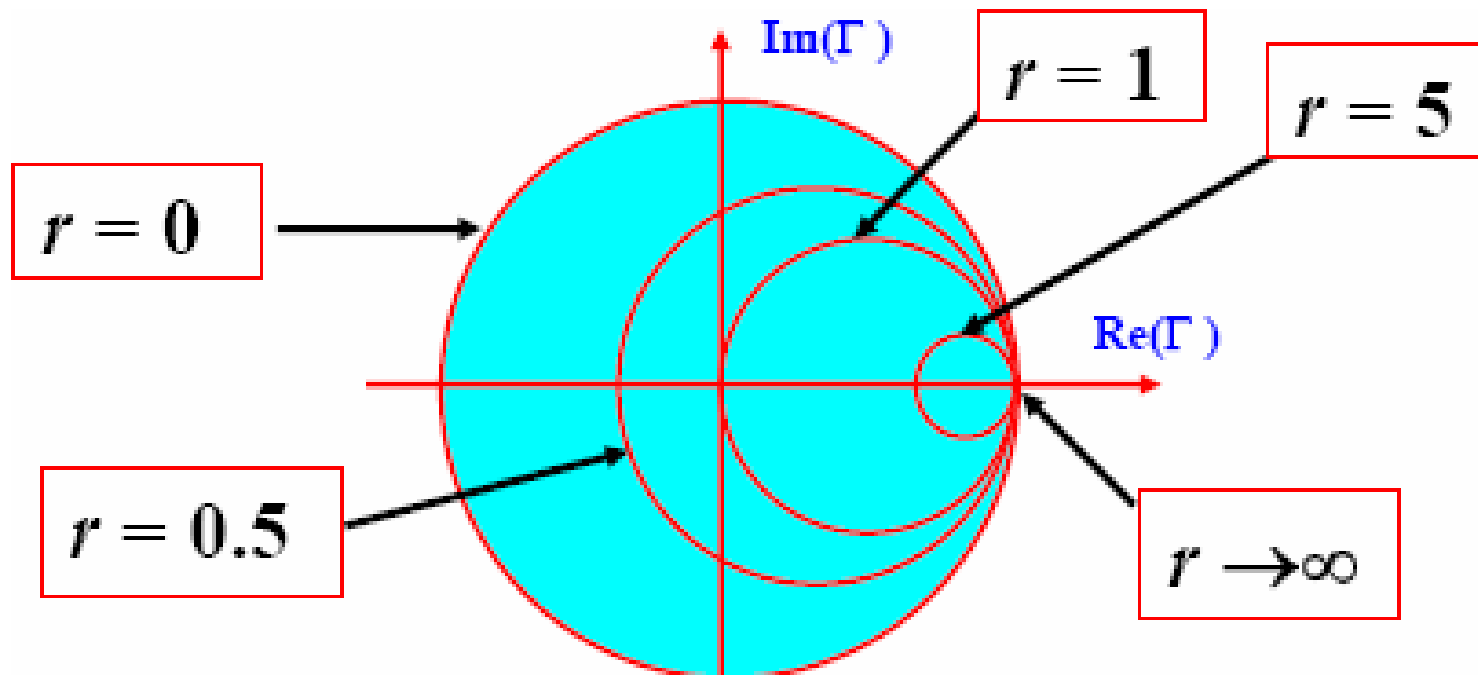

$$\text{Center} = \left\{ \frac{r}{1+r}, 0 \right\}$$

$$\text{Radius} = \frac{1}{1+r}$$

Smith Chart Circle Equations




$$\left(\Gamma_r - \frac{r_L}{1 + r_L}\right)^2 + \Gamma_i^2 = \left(\frac{1}{1 + r_L}\right)^2,$$
$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x_L}\right)^2 = \left(\frac{1}{x_L}\right)^2$$


The result for the **imaginary part** indicates that on the complex plane with coordinates $(\text{Re}(\Gamma), \text{Im}(\Gamma))$ all the possible impedances with a given normalized reactance **x** are found on a **circle** with

$$\text{Center} = \left\{ 1, \frac{1}{x} \right\} \qquad \text{Radius} = \frac{1}{x}$$

As the normalized reactance **x** varies from $-\infty$ to ∞ , we obtain a family of arcs contained inside the domain of the reflection coefficient **$|\Gamma| \leq 1$** .

x-circles

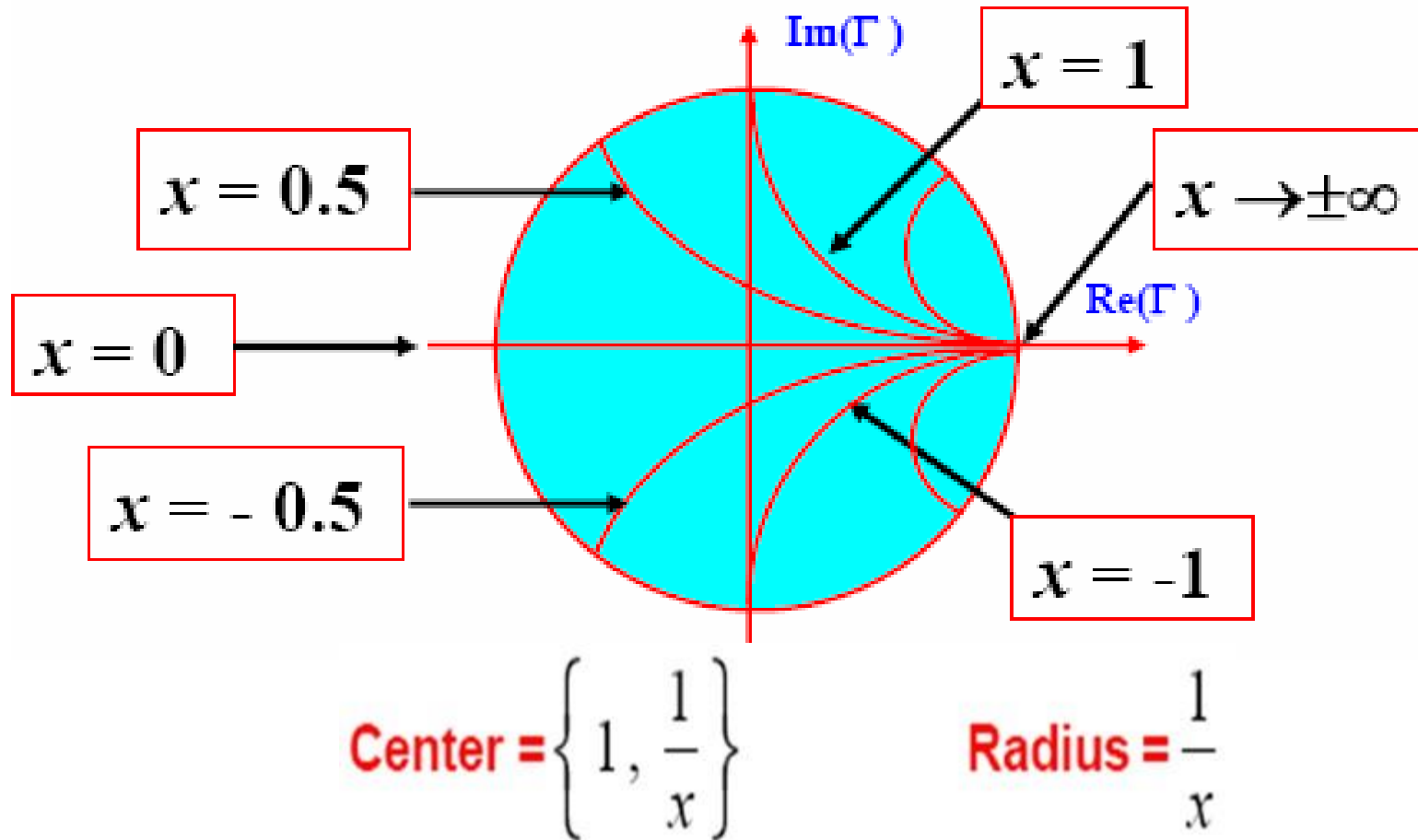


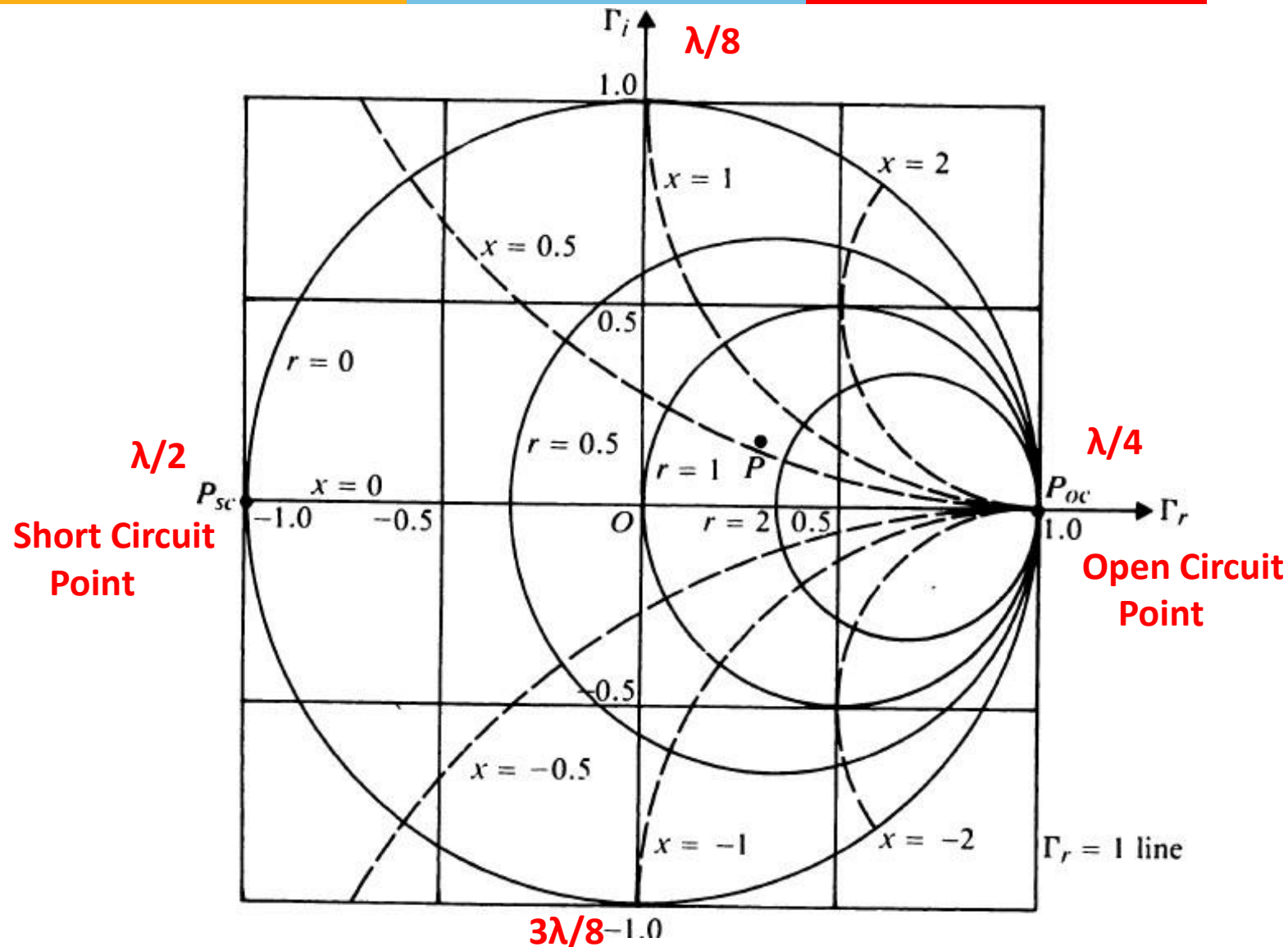

Important points about Smith chart




- Impedance divided by line impedance (50 Ohms)
 - $Z1 = 100 + j50$
 - $Z2 = 75 - j100$
 - $Z3 = j200$
 - $Z4 = 150$
 - $Z5 = \text{infinity}$ (an open circuit)
 - $Z6 = 0$ (a short circuit)
 - $Z7 = 50$
 - $Z8 = 184 - j900$
- Then, normalize and plot. The points are plotted as follows:
 - $z1 = 2 + j$
 - $z2 = 1.5 - j2$
 - $z3 = j4$
 - $z4 = 3$
 - $z5 = \text{infinity}$
 - $z6 = 0$
 - $z7 = 1$
 - $z8 = 3.68 - j18S$

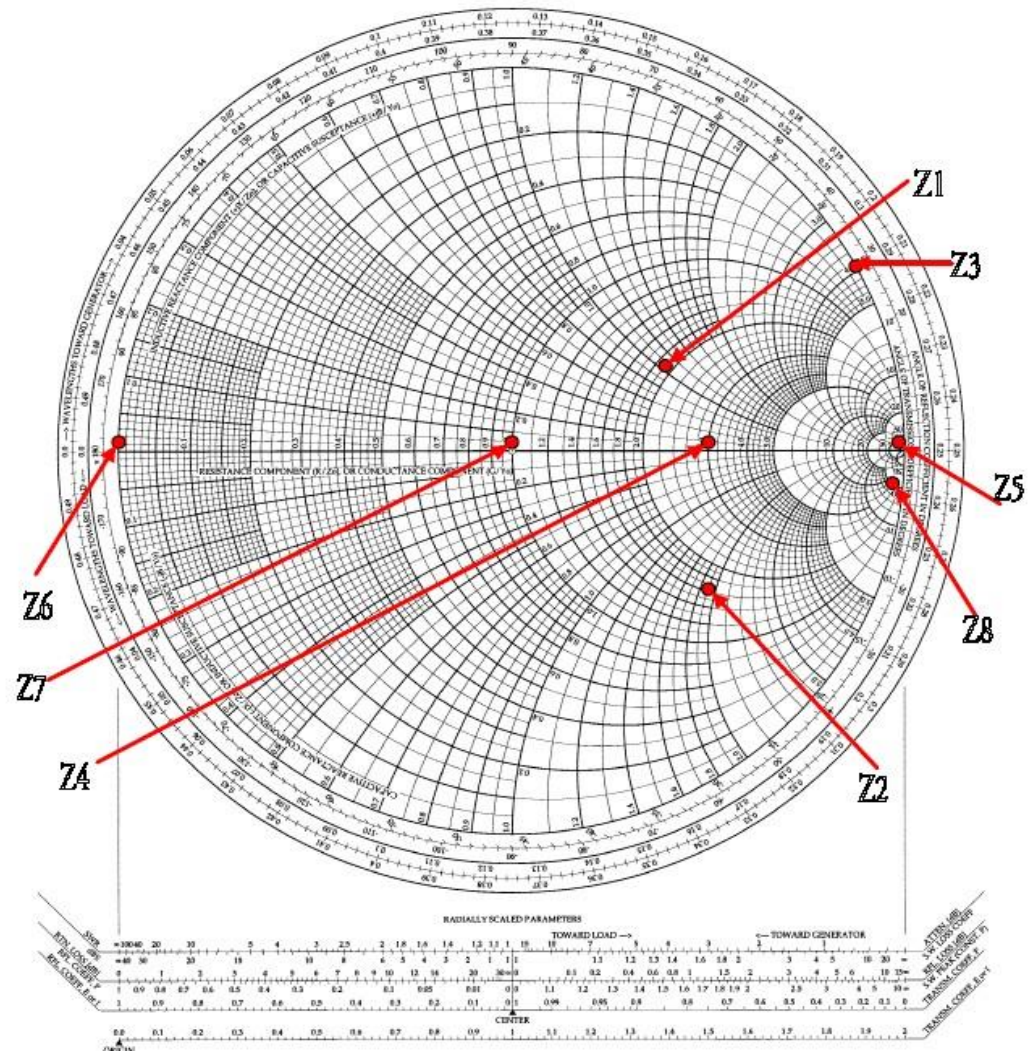

innovate achieve lead



Away from Load: Clockwise

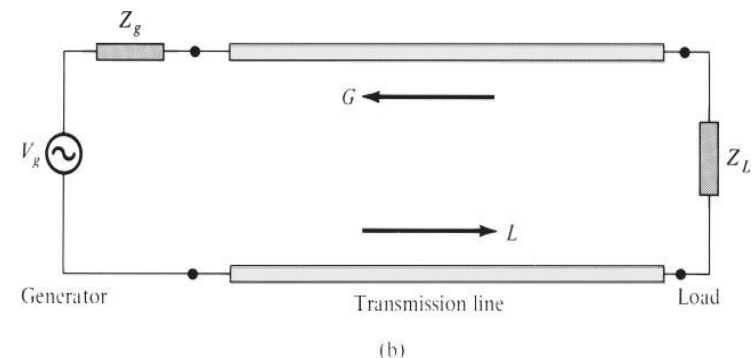

Plotting a constant VSWR circle

Step1: Locate the normalized load impedance on the chart (say P)

achieve lead

Step3: The value of r at this point gives you SWR 's'

Constant VSWR Circle

P

S value

O

Toward Generator

Away From Generator

Step2: Take center of the Smith chart (O) as the center and the radius as OP and draw a circle. (The circle passes through the normalized load impedance).

Learning Example




Find the input impedance of a section of a $50\ \Omega$ loss-less transmission line that is 0.1λ long and is terminated in a short circuit.

Learning Example

innovate

achieve

lead

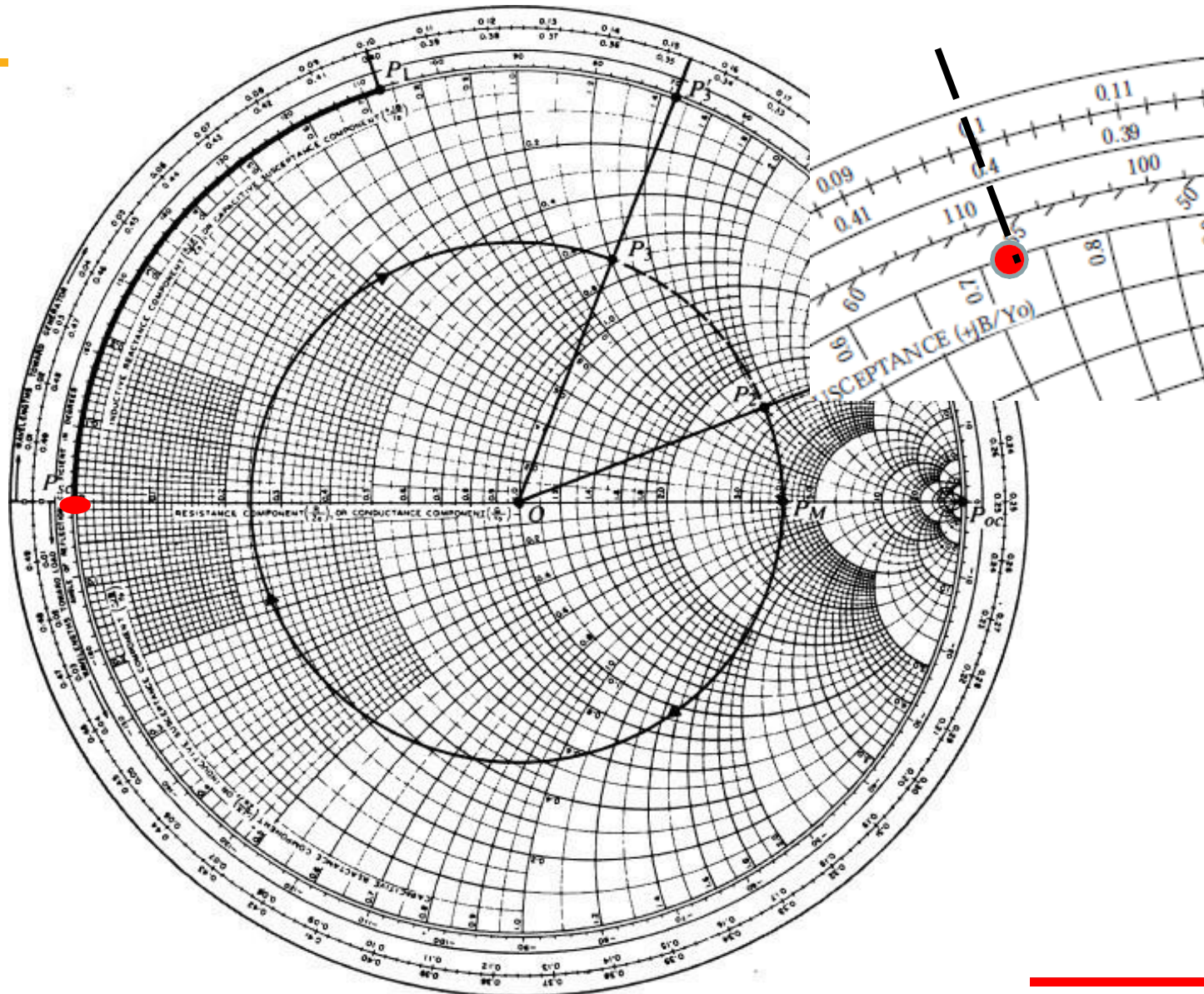

To find the reflection coefficient for a known load

1. Normalization

$$\begin{aligned} z_n &= (25 + j\ 100)/50 \\ &= 0.5 + j\ 2.0 \end{aligned}$$

3. Find normalized reactance arc

$$x = 2.0$$

2. Find normalized resistance circle


$$r = 0.5$$

4. This vector represents the reflection coefficient

$$\Gamma = 0.52 + j0.64$$

$$|\Gamma| = 0.8246$$
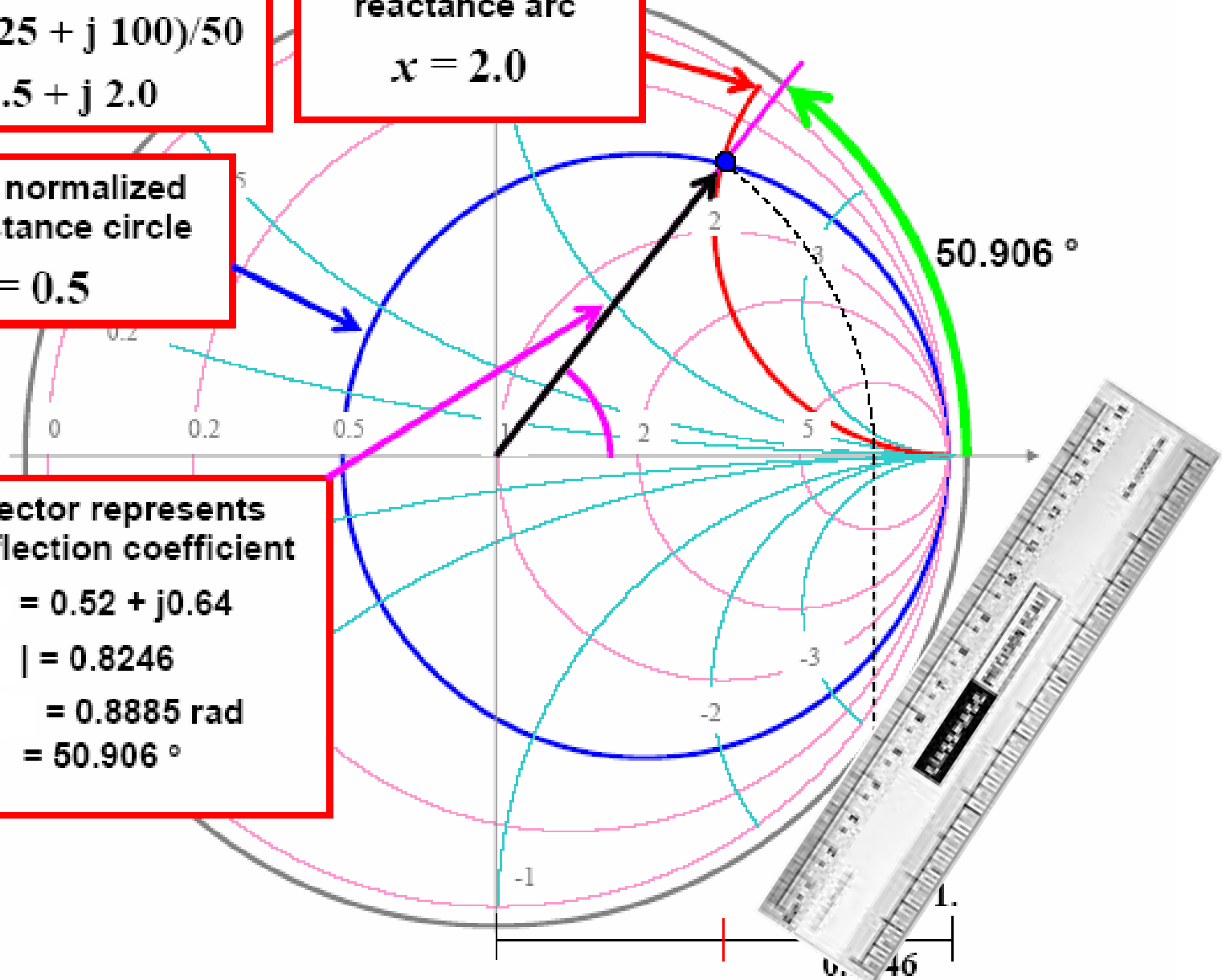
$$\begin{aligned} \angle \Gamma &= 0.8885 \text{ rad} \\ &= 50.906^\circ \end{aligned}$$



Example




A lossless transmission line with a characteristic impedance of 50Ω is terminated in a load impedance $40 + j30 \Omega$. Using Smith Chart techniques, determine:

- The reflection coefficient Γ (magnitude and phase), and the VSWR
- The input impedance seen looking into the line if it is 0.2λ long.
- The length of line needed to make the input impedance look real (one solution is sufficient), and the associated resistance value.

a) $\Gamma = j0.333 = 0.333\angle 90^\circ$

$$z_L = \frac{Z_L}{Z_0} = 0.8 + j0.6.$$

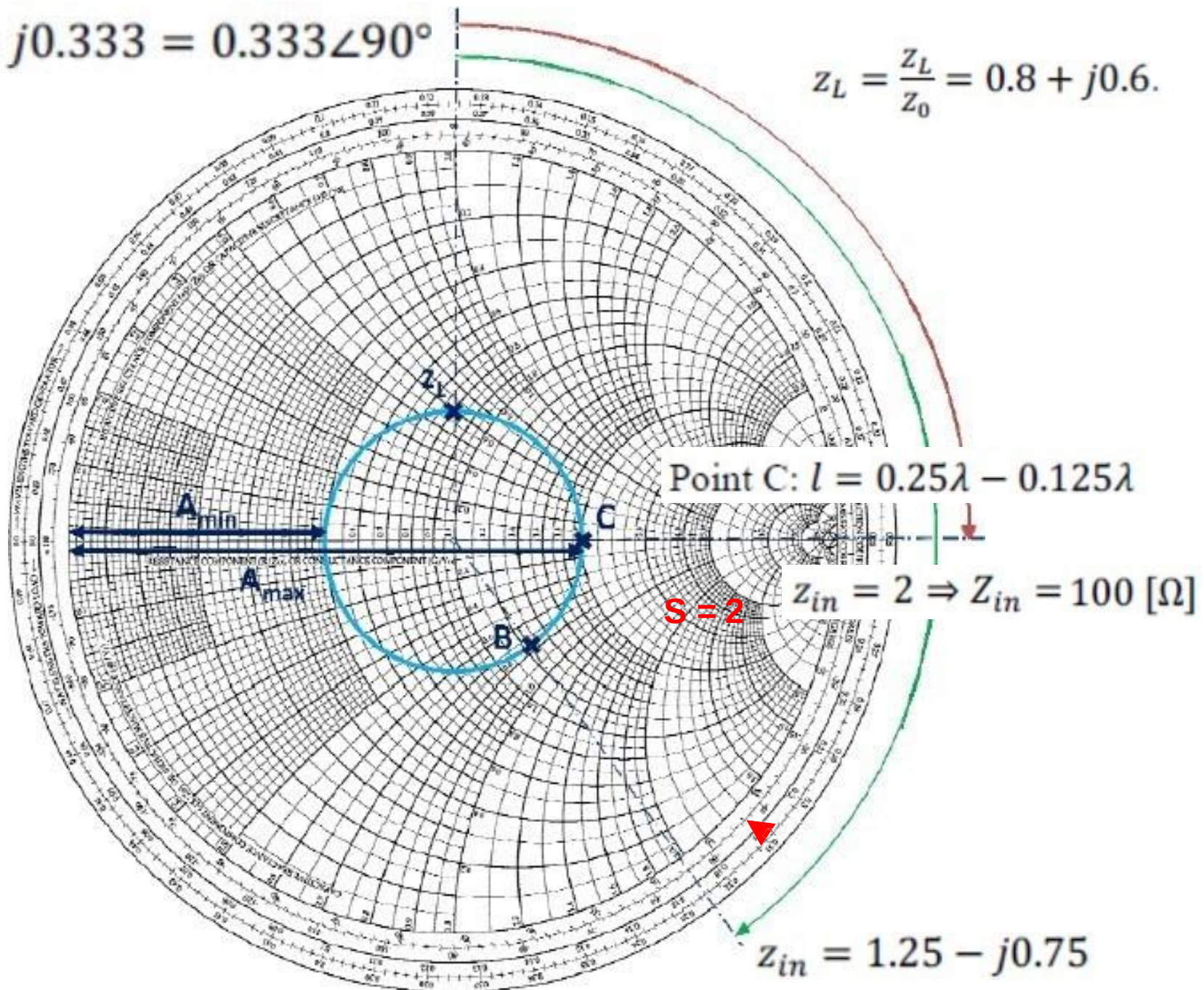


Example

EXAMPLE 9–14 A lossless transmission line of length 0.434λ and characteristic impedance $100\ \Omega$ is terminated in an impedance $260 + j180\ \Omega$. Find (a) the voltage reflection coefficient, (b) the standing-wave ratio, (c) the input impedance, and (d) the location of a voltage maximum on the line.

$$z' = 0.434\lambda,$$

$$R_0 = 100\ \Omega,$$

$$Z_L = 260 + j180$$

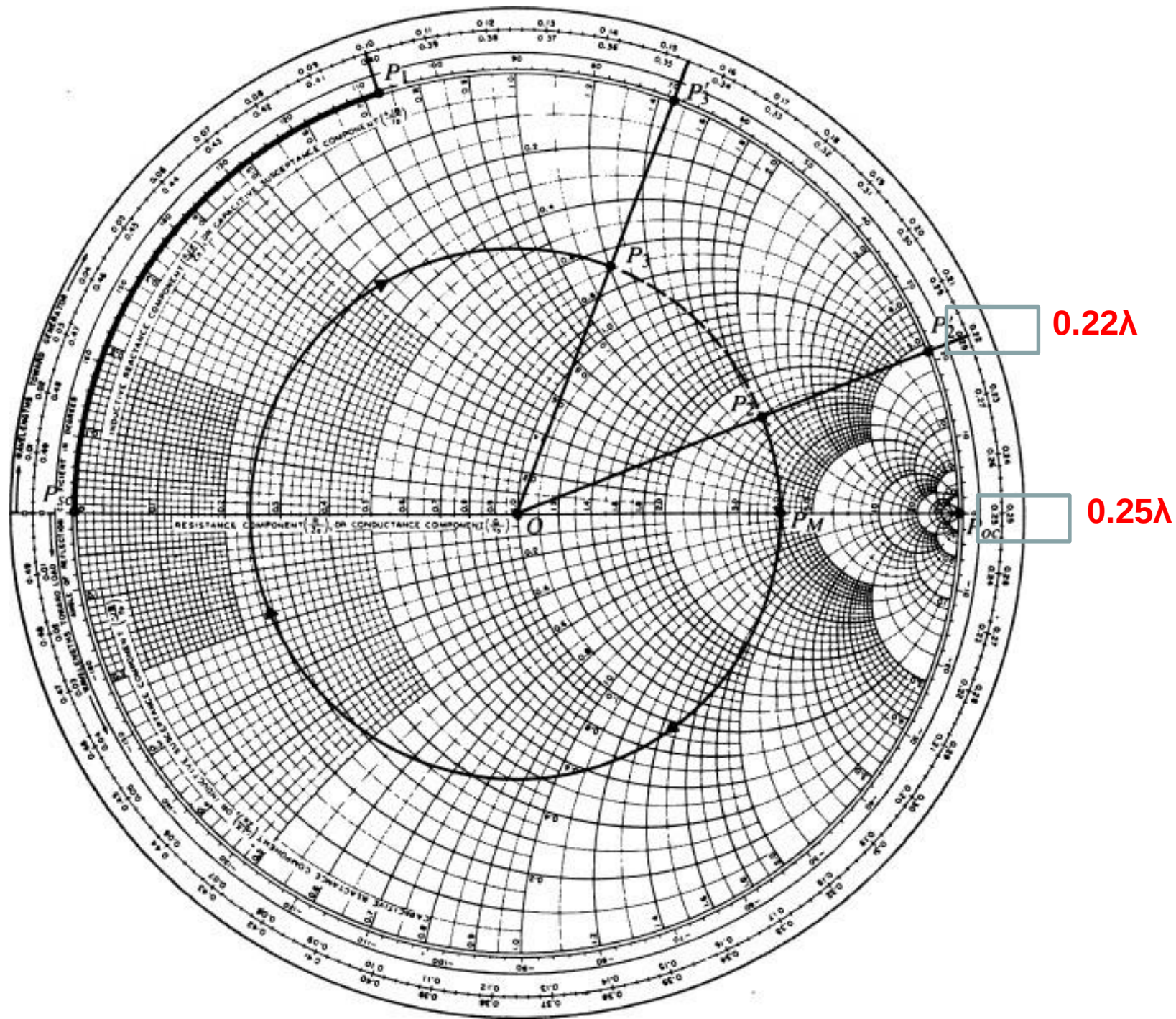

Why Impedance Matching



- **Malfunctioning of the source**
- **Breakdown (High VSWR)**
- **Frequency Pulling**


Sol: Impedance Matching

Impedance Matching




lossless


Z_L is resistive

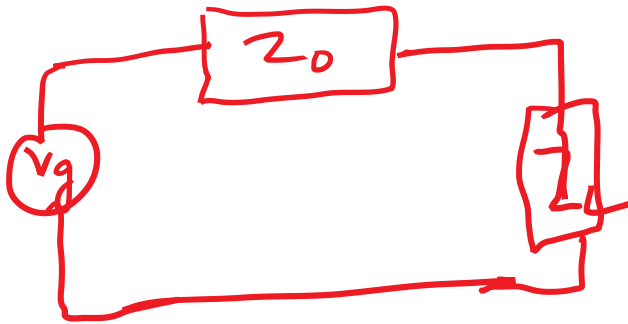

$$Z_0 \neq Z_L \rightarrow$$

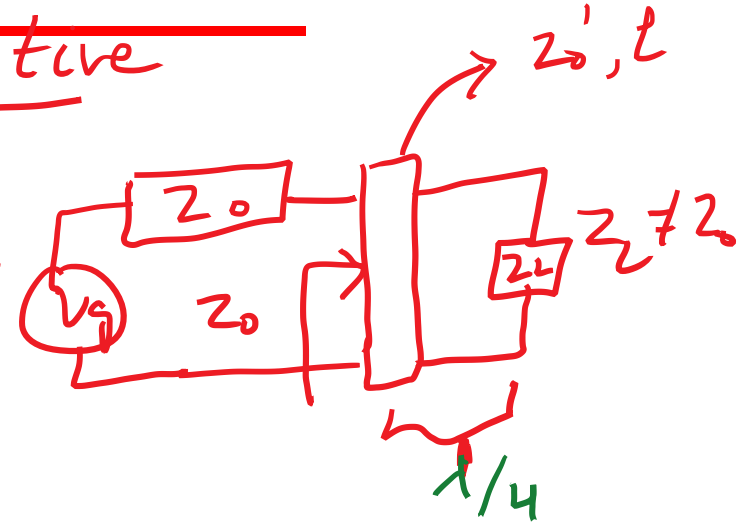

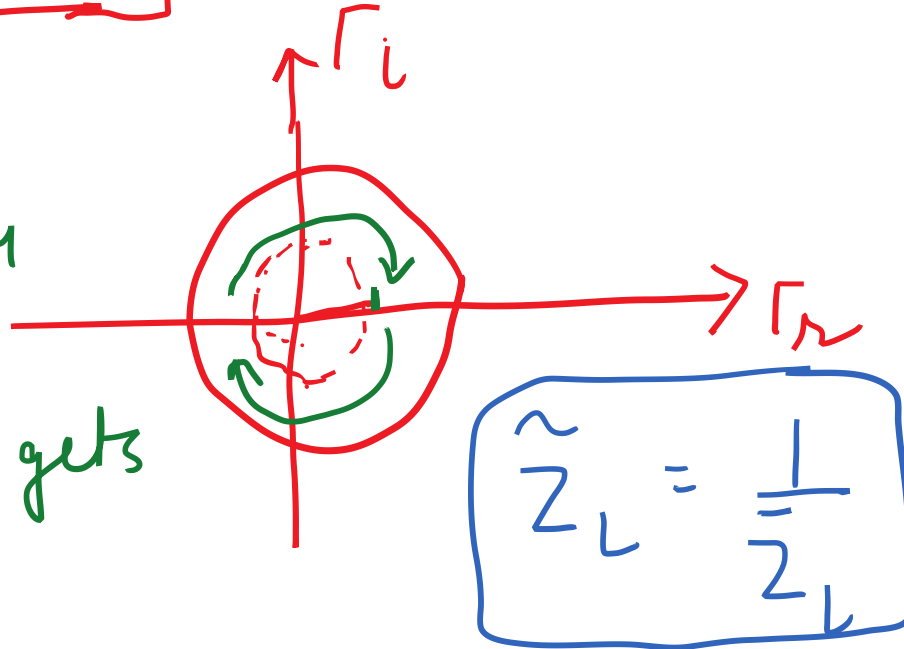At every $\lambda/4$
Normalized
impedance
inverted
gets



Resistive
to
Resistive
matching


Impedance Matching



Quarter Wave Transformer

lossless

Z_L is resistive

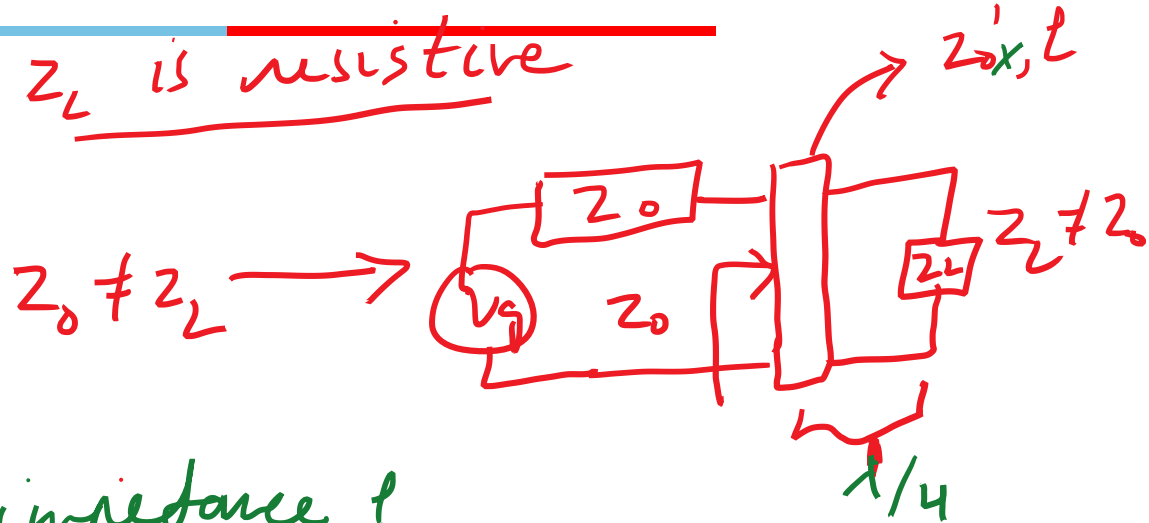

$l = \lambda/4$

Normalized load impedance l

$\frac{Z_L}{Z_0} \xrightarrow{\text{after } \lambda/4} \left(\frac{Z_0 x}{Z_L} \right)$ Normalized Resistive value to


So Actual impedance $\rightarrow \frac{Z_0 x}{Z_L} \cdot Z_0$ Resistive matching

For matching $\rightarrow \left[Z_0 = \frac{Z_0 x^2}{Z_L} \right]$ so $\left[Z_0 x = \sqrt{Z_0 Z_L} \right]$

Quarter Wave Transformer



What about complex impedances??

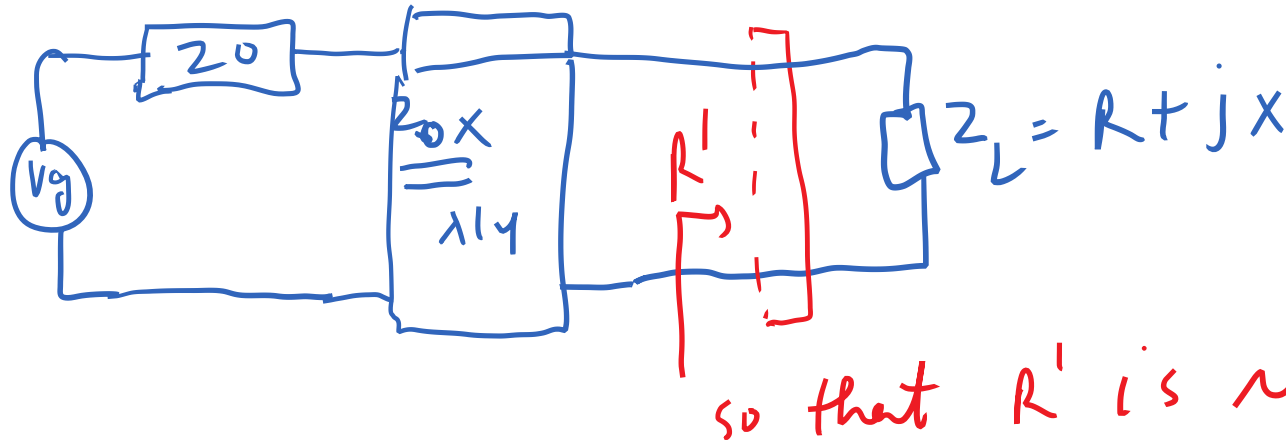


Is sweet ✓ $Z_o X$ for every value not available
✓ single frequency use

Example



Match the following load impedance to
 $Z_0 = 50 \Omega$ line

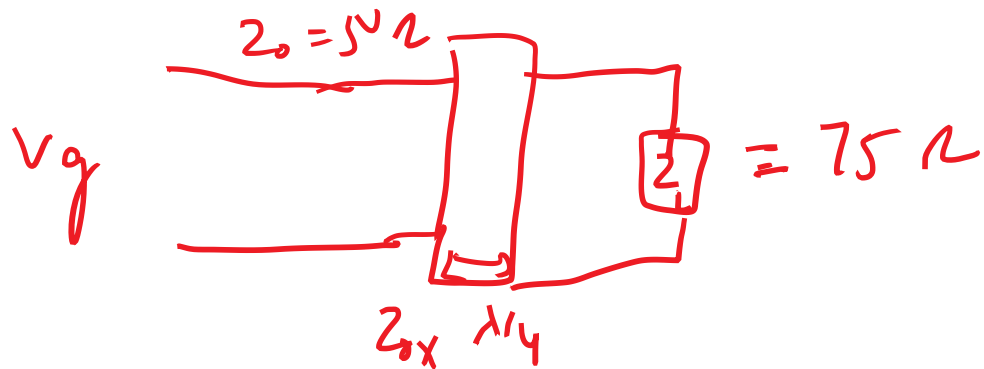a) $Z_L = 75 \Omega$ b) $Z_L = 100 + j75 \Omega$




$$\text{Sol}^n \quad Z_{0x} = \sqrt{75 \times 50}$$

at $\frac{\lambda}{4}$

$$Z_{0x} = 61.23 \Omega$$

Example

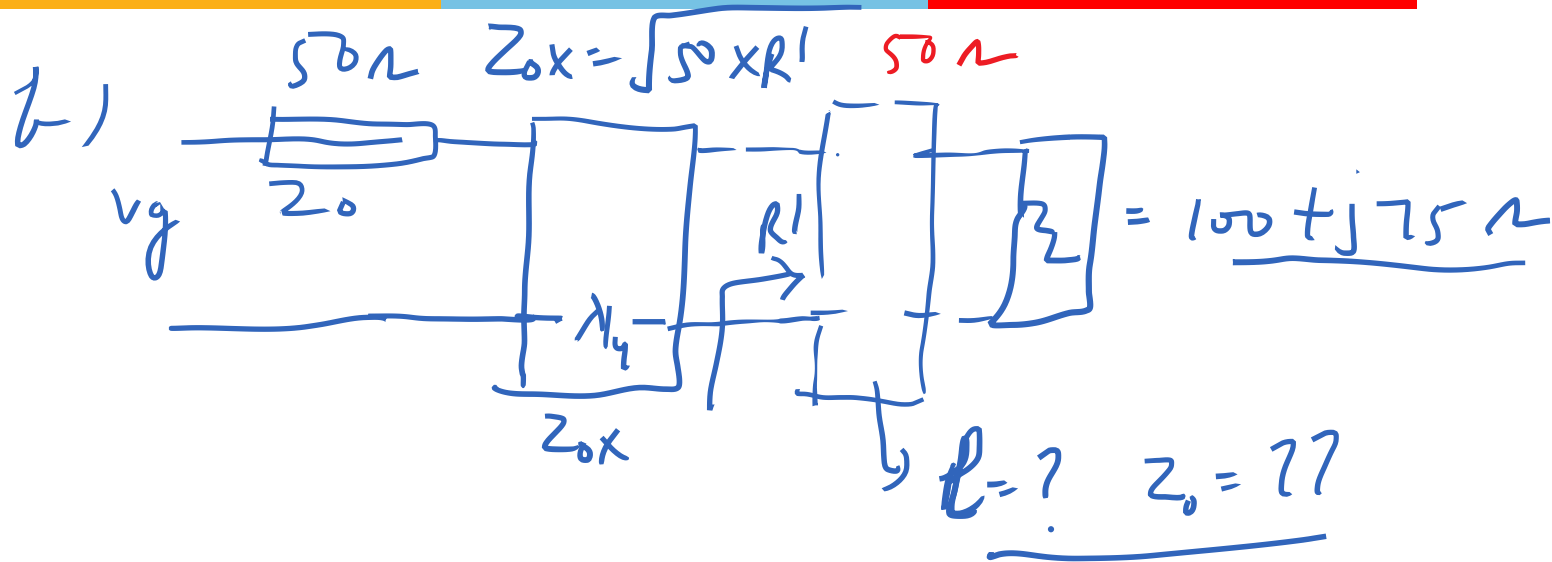


$$Z_1' = 2 + 1.5j$$

→ Draw on Smith chart and

find the value of l at which impedance is real.

Example

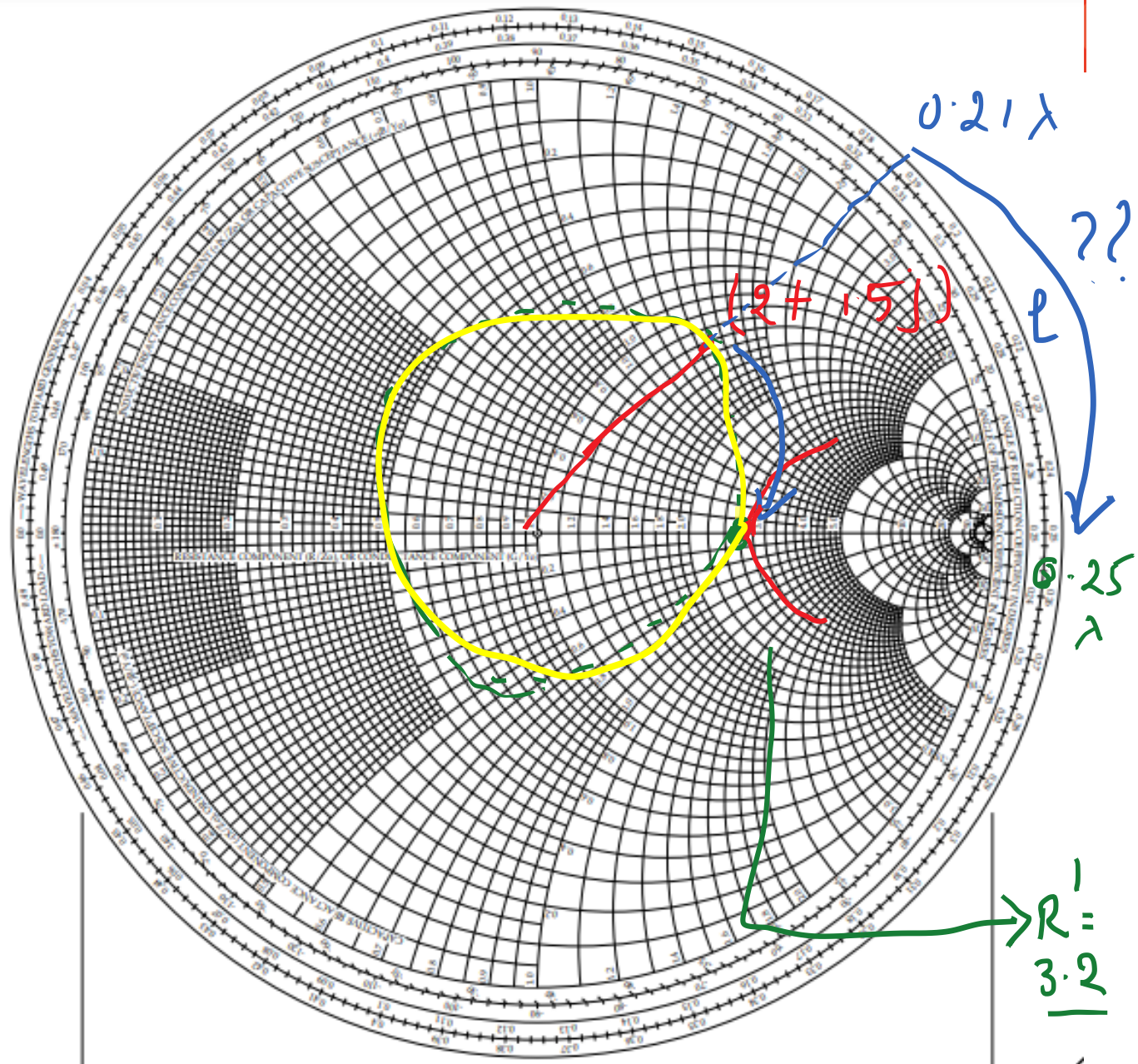


Impedance Matching with stub



Stub : A short section of transmission line

- Single Stub
- Double Stub

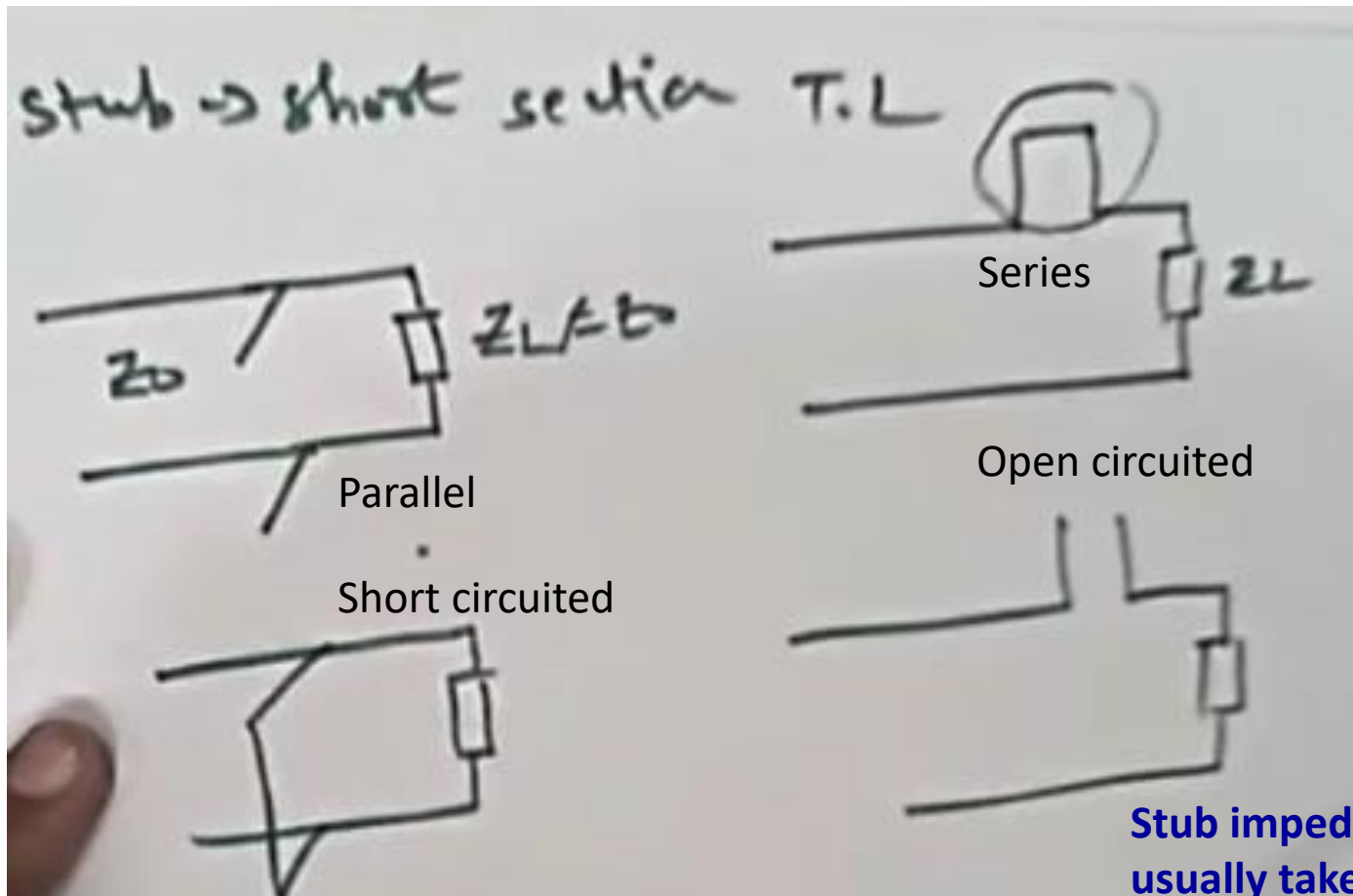

Stub impedance is usually taken as characteristic impedance of transmission line

To find the admittance for a known load

$$Z_L = 30 + j70$$



Step1:

Normalized impedance

step2

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma_L = \frac{\tilde{Z}_L - 1}{\tilde{Z}_L + 1}$$


$$\begin{aligned} \Gamma_L &= \frac{Y_0 - Y_L}{Y_0 + Y_L} \\ &= \frac{1 - \tilde{Y}_L}{1 + \tilde{Y}_L} \end{aligned}$$

$$\Gamma_L = -\frac{(\tilde{Y}_L - 1)}{(\tilde{Y}_L + 1)}$$

$$[\gamma = g + jb]$$

Y_B

$$Y = Y_0 Y_B = Y_B / Z_0$$



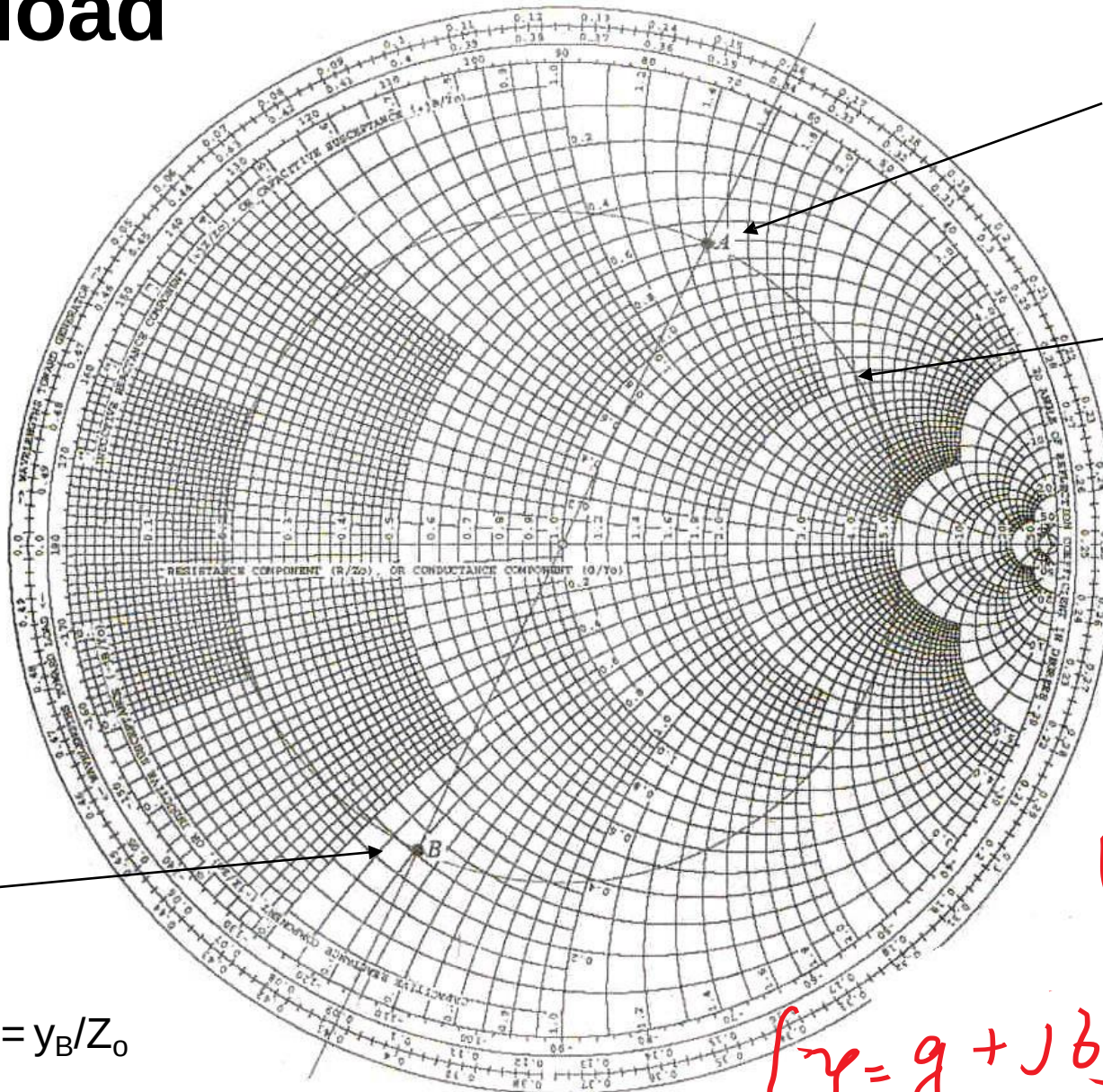


Parallel Single stub (open circuited)

innovate

achieve

lead

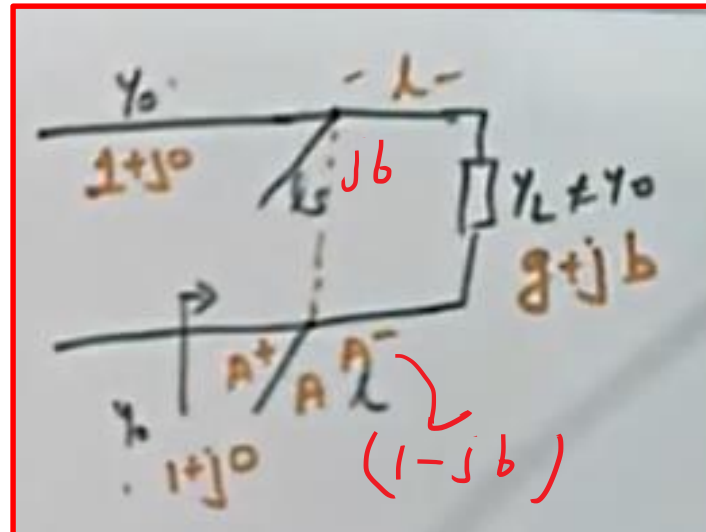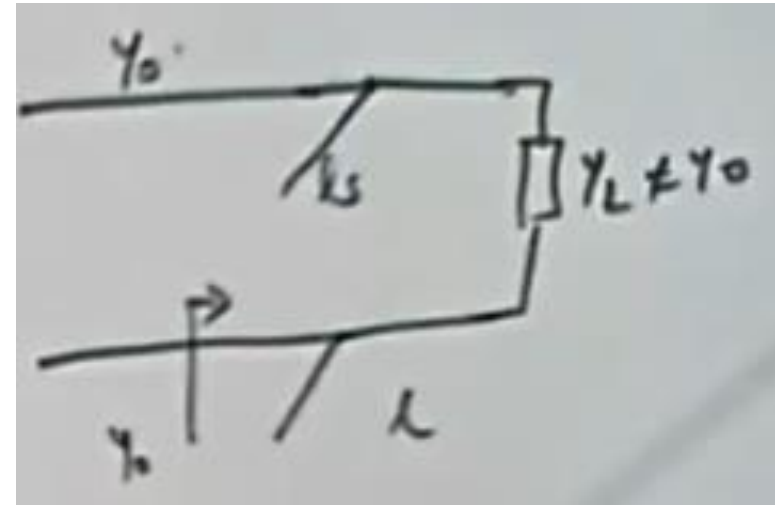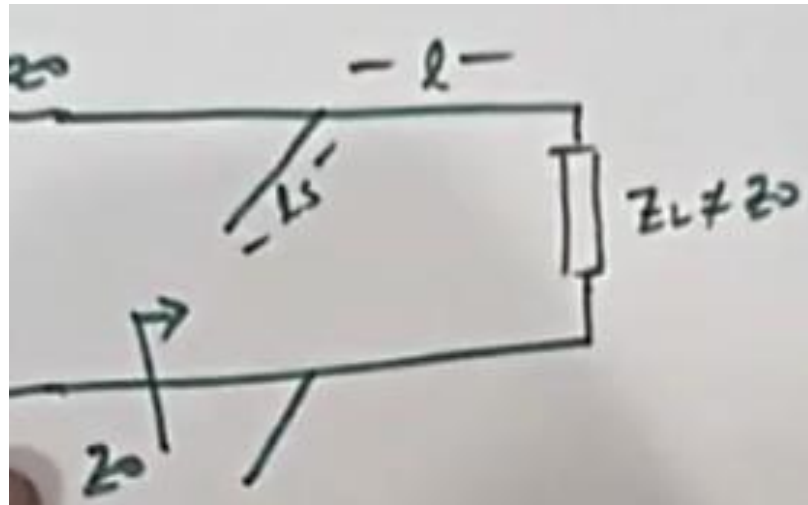

$$Z_{oc} = -jZ_0 \cot \beta L$$

$$Y_{oc} = \frac{j \tan \beta L}{Z_0}$$


$$Z_{sc} = jZ_0 \tan \beta L$$

$$Y_{sc} = \frac{-j \cot \beta L}{Z_0}$$


Example



$$\tilde{Z}_L = 0.2 - j0.5$$

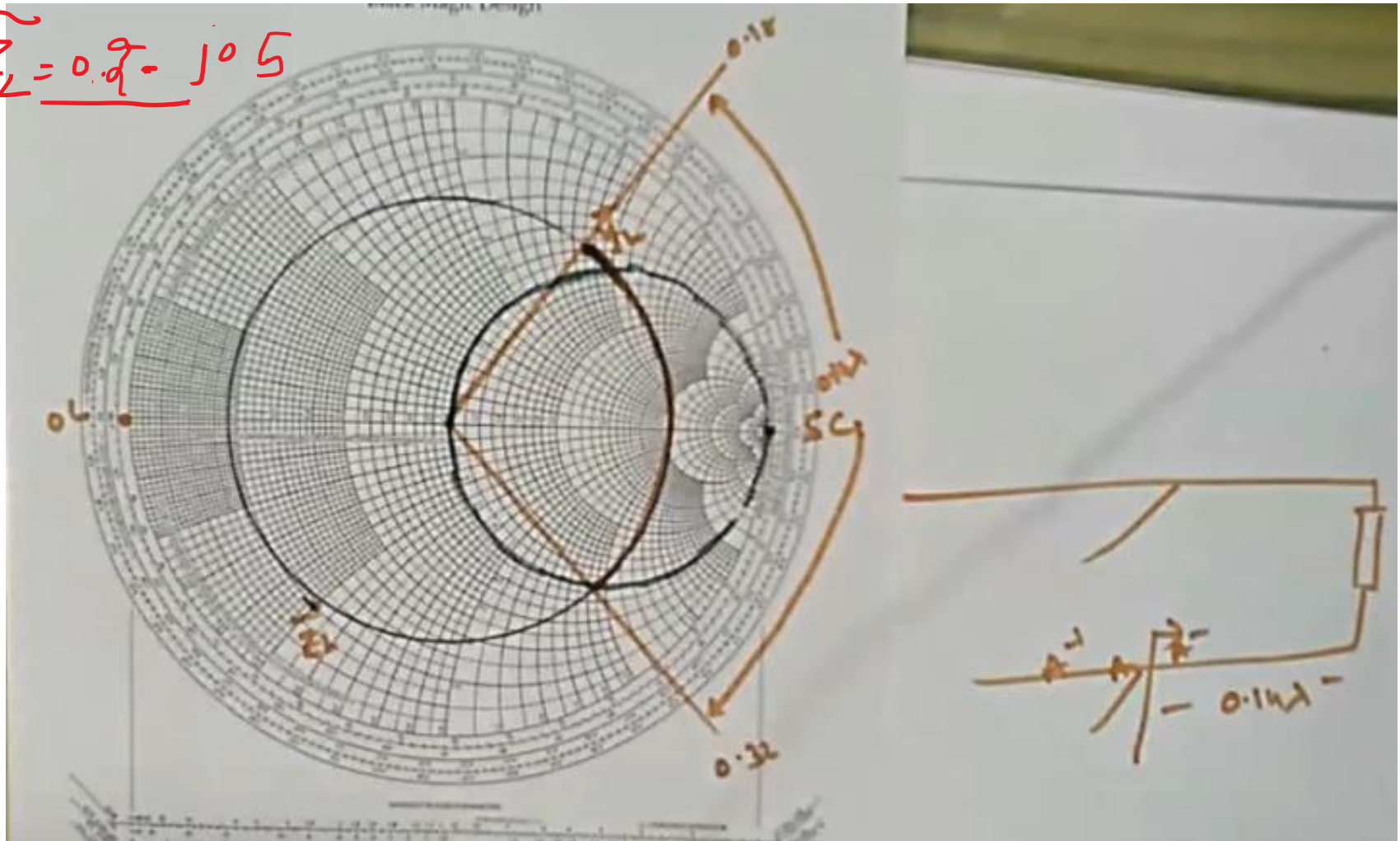

Example

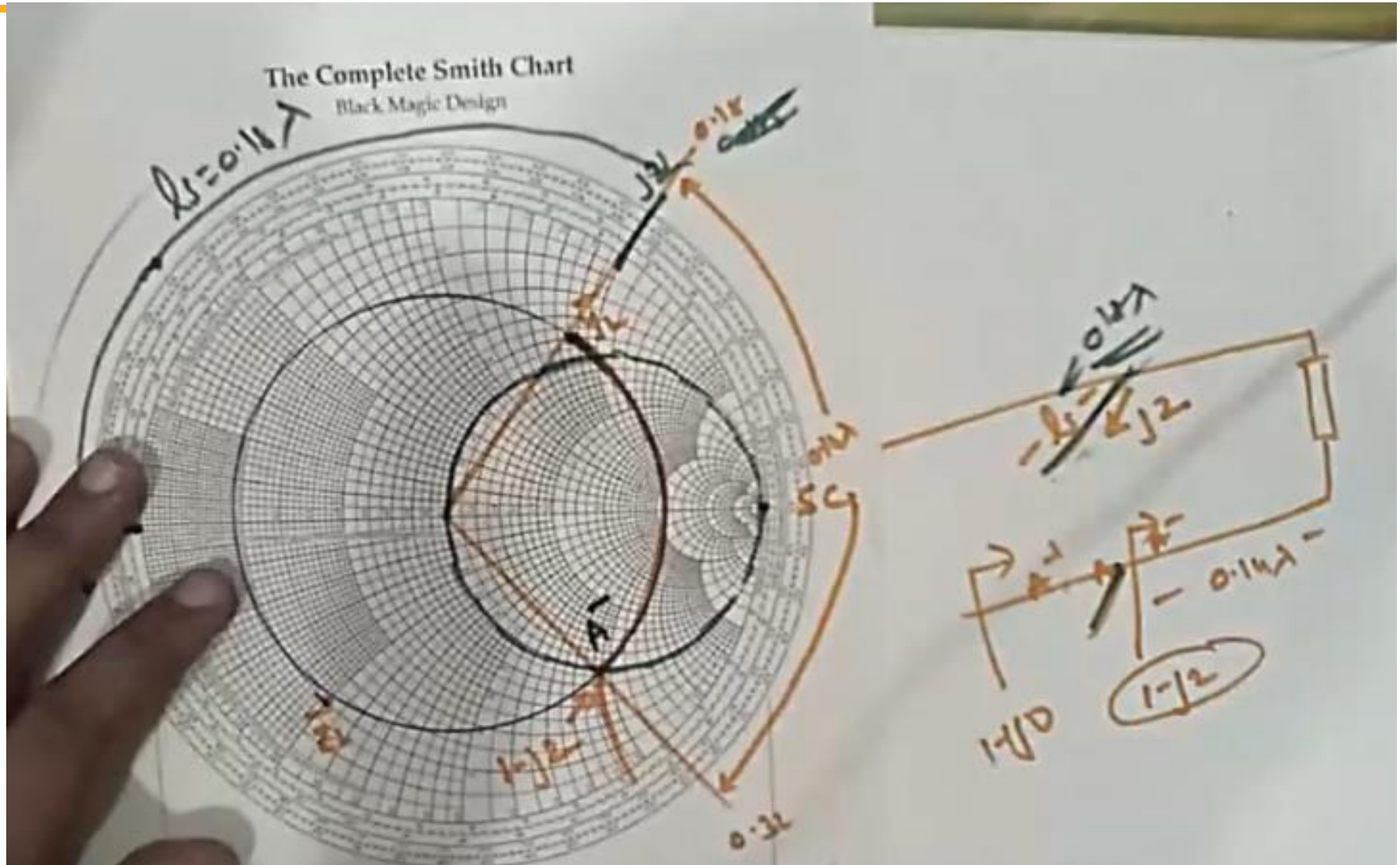


Parallel Double stub (Short circuited)

innovate

achieve

lead

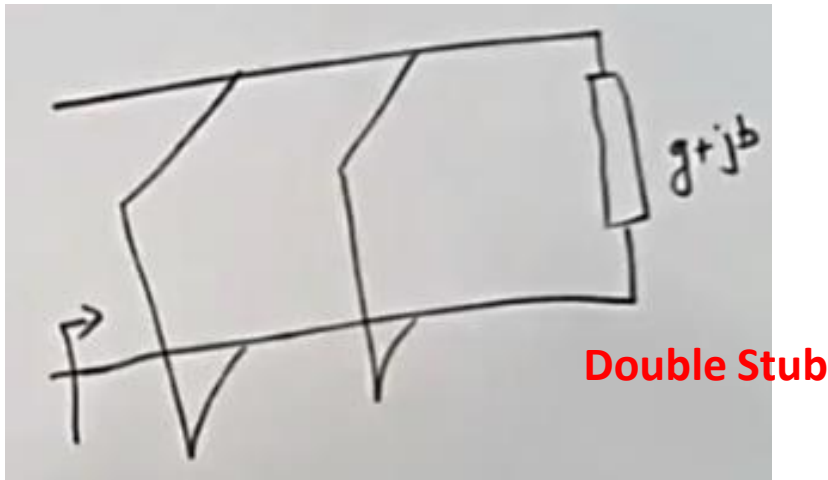
What if the Load is continuously changing?



$$\frac{3\lambda}{8}$$

$$2\beta l = 2 \times 2\pi \times \frac{3\lambda}{8} \times \frac{1}{\lambda}$$

$$= 2.75$$


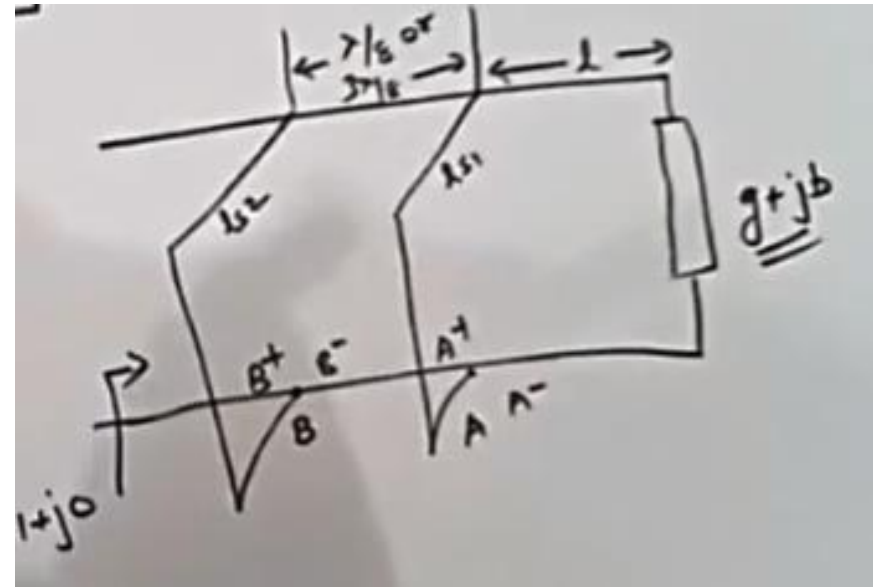


Parallel Double stub (Short circuited)

innovate

achieve

lead

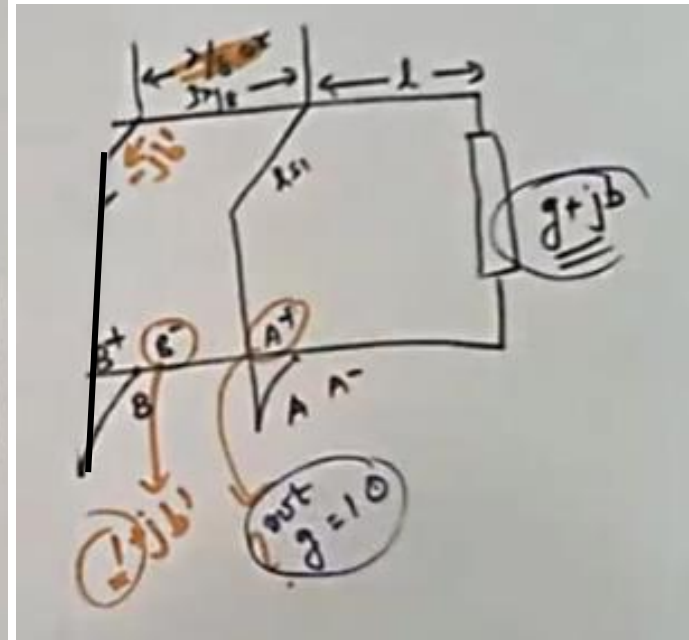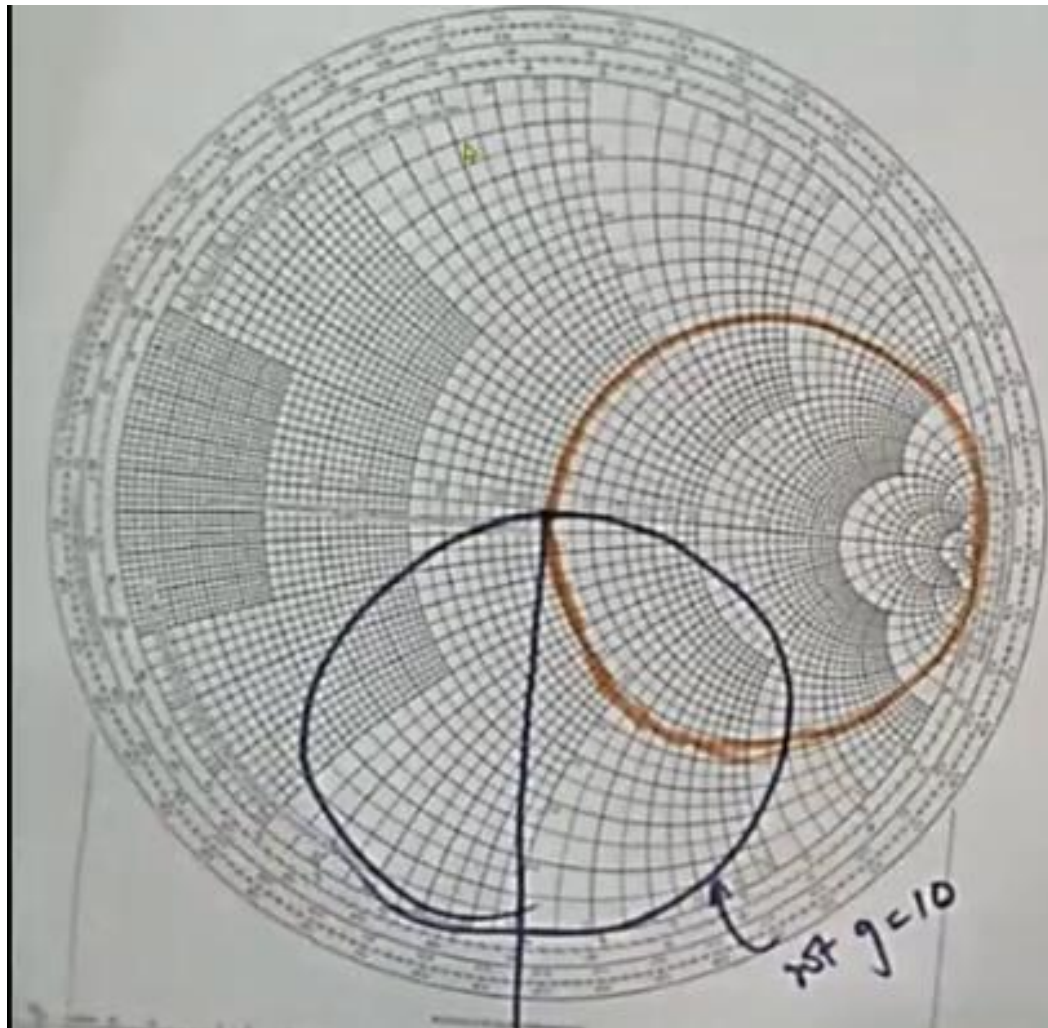


Parallel Double stub (Short circuited)

innovate


achieve

lead

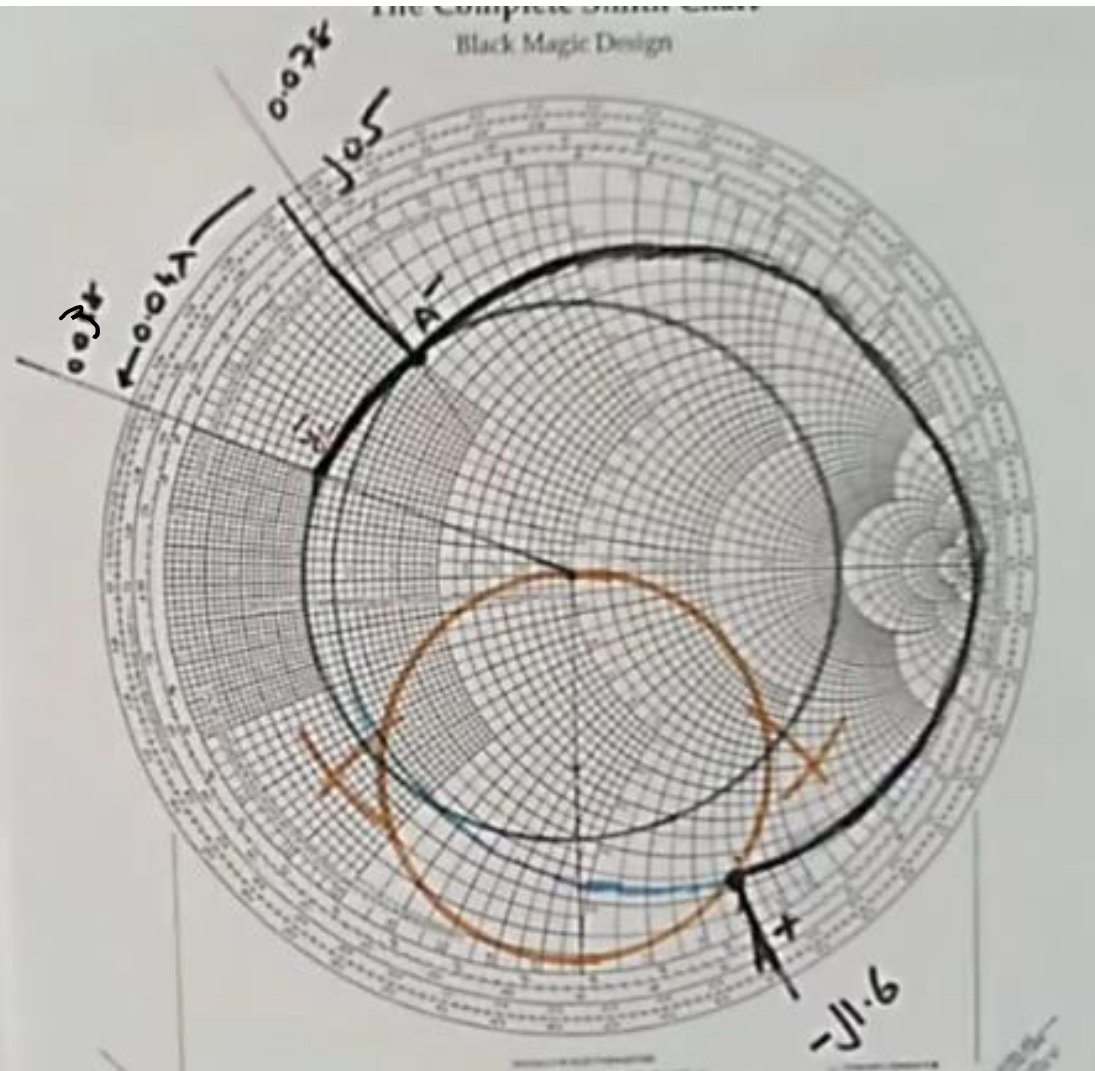

$$\tilde{Z}_L = 2.5 - j2.5$$


$$\tilde{Y}_L = 0.2 + j0.2$$

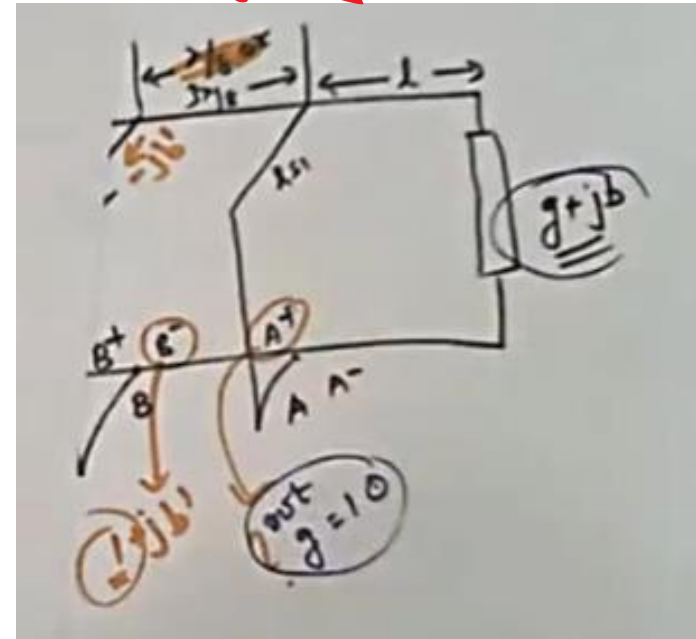


$$j0.5 + \text{stub} = -j1.6$$

$$\text{stub} = -2.11 \checkmark$$


circuited)
innovate achieve lead

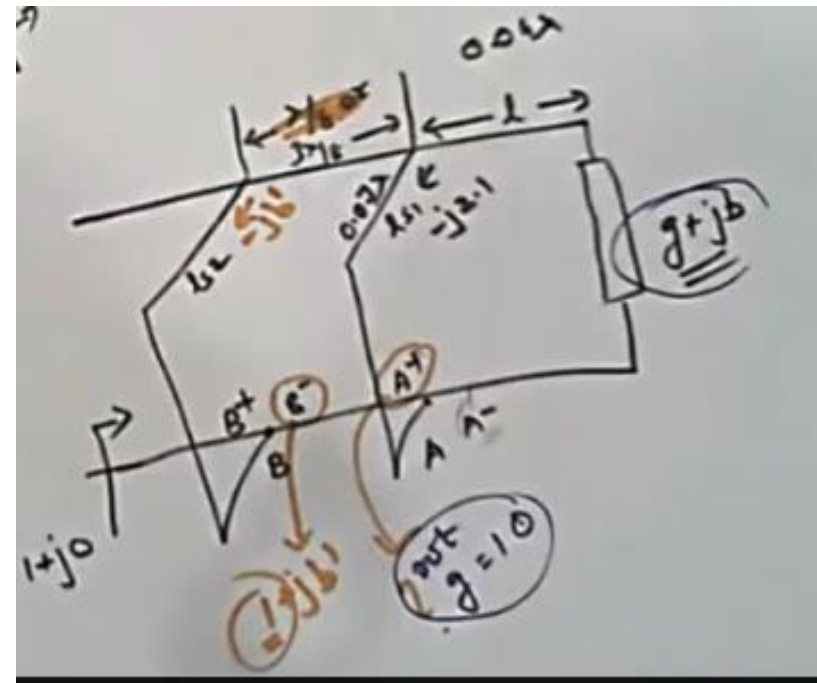


lead

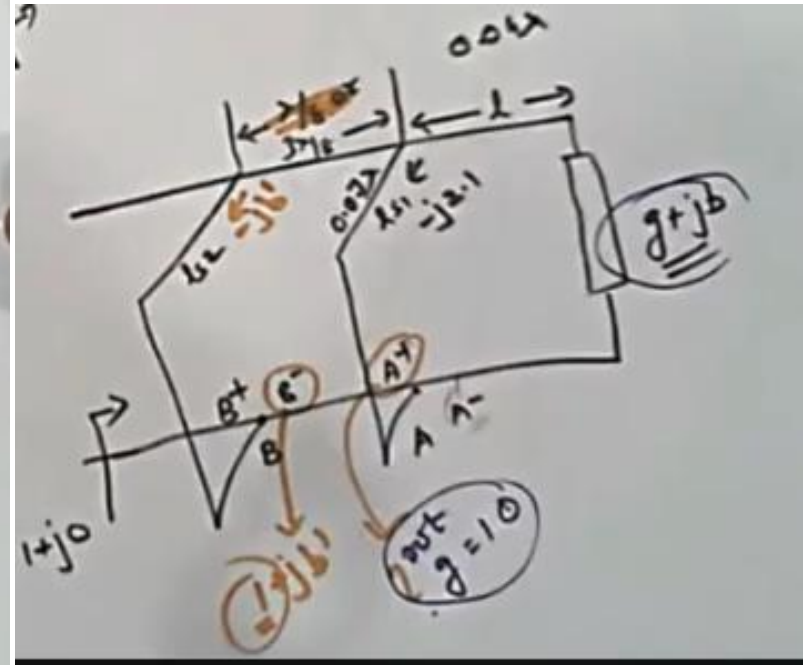


lead

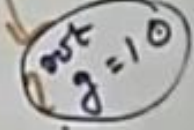

Microstrip Line (Planar)

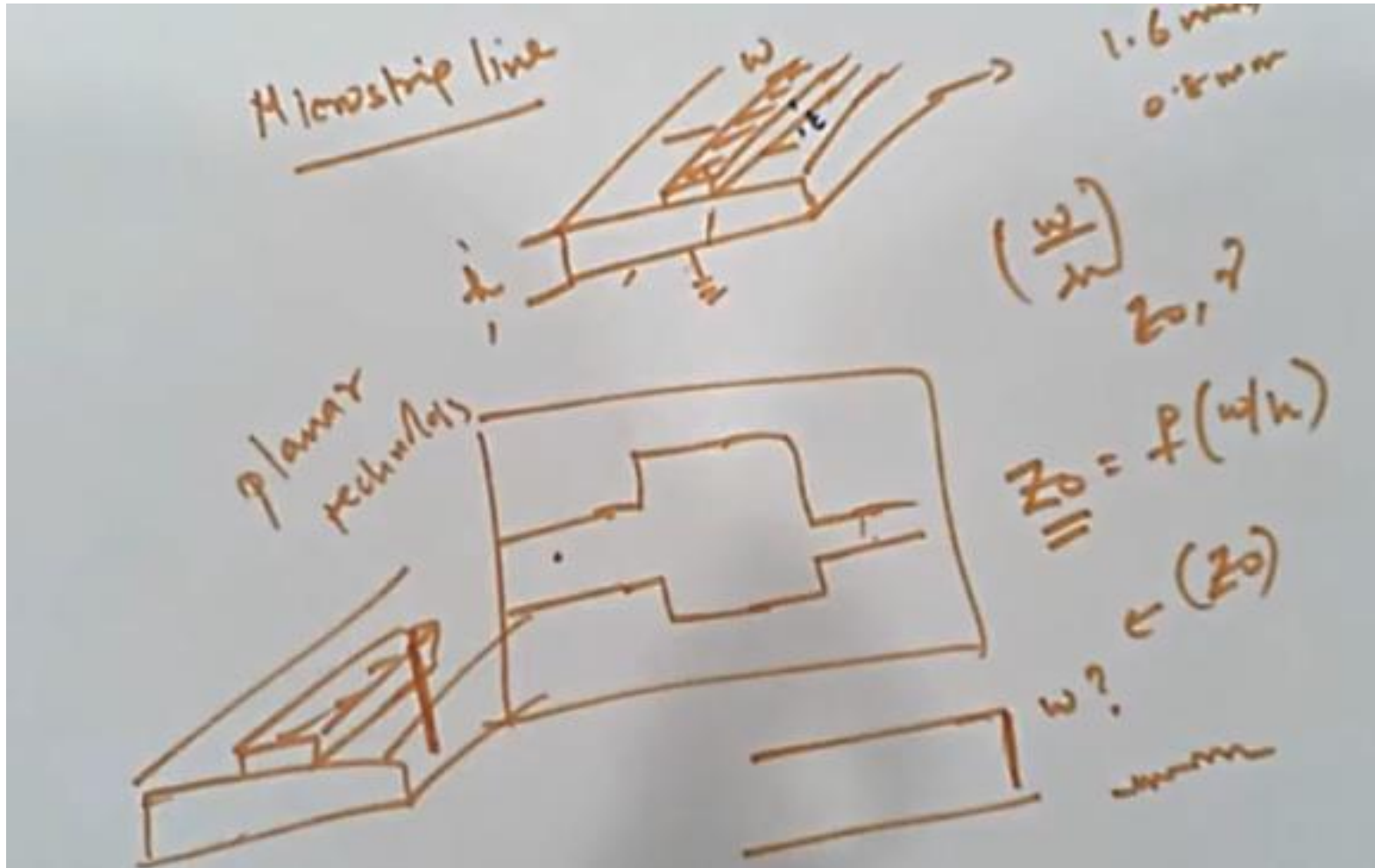

Microstrip Line

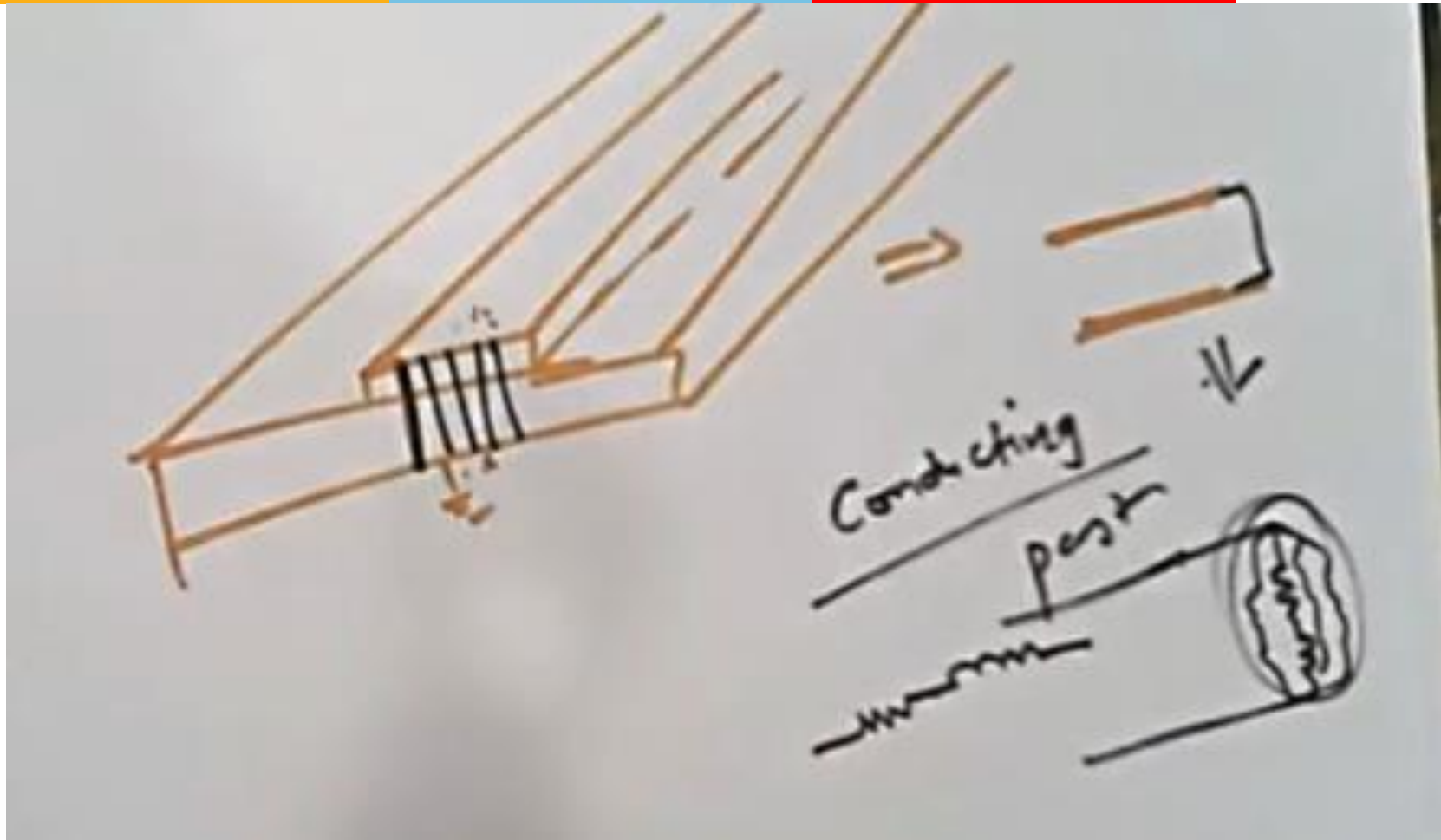

Power Relations



Power relations

Z_s , Z_0 , Z_L , Z_{in} , Γ

Z_s , Z_L

$$P = \text{Re}\{VI^*\}$$

peak values

$$V = \frac{V_{in}^+}{2} + \frac{V_{in}^-}{2} = \frac{V_{in}^+}{2}(1 + \Gamma_{in})$$

$$I = \frac{V_{in}^+}{Z_0} - \frac{V_{in}^-}{Z_0} = \frac{V_{in}^+}{Z_0}(1 - \Gamma_{in})$$

$$P = \frac{1}{2} \left[\frac{(V_{in}^+)^2}{Z_0} (1 - |\Gamma_{in}|^2) \right] = P_{av}$$